




# **Elektroakustika**

## **L10: Reprodukčné systémy**

**doc. Ing. Jozef Juhár, PhD.**


**<http://voice.kemt.fei.tuke.sk>**

# Nízkotónový reproduktor

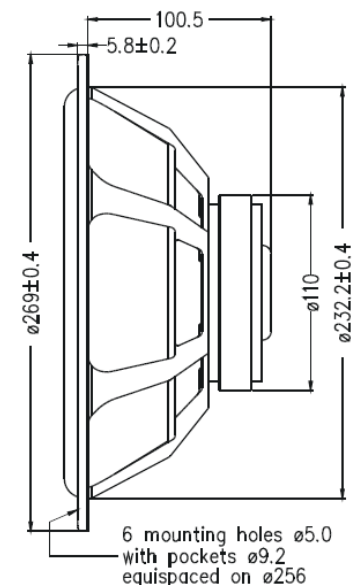

Nominal Impedance	8 Ohms	Voice Coil Resistance	6.1 Ohms
Recommended Frequency Range	30 - 1500 Hz	Voice Coil Inductance	3.08 mH
Short Term Power Handling *	300 W	Force Factor	11.6 N/A
Long Term Power Handling *	80 W	Free Air Resonance	25 Hz
Characteristic Sensitivity (2.83V, 1m)	91 dB	Moving Mass	38.5 g
Voice Coil Diameter	39 mm	Air Load Mass In IEC Baffle	3.8 g
Voice Coil Height	14 mm	Suspension Compliance	1.1 mm/N
Air Gap Height	6 mm	Suspension Mechanical Resistance	1.66 Ns/m
Linear Coil Travel (p-p)	8 mm	Effective Piston Area	350 cm <sup>2</sup>
Maximum Coil Travel (p-p)	20 mm	VAS	164 Litres
Magnetic Gap Flux Density	0.9 T	QMS	3.99
Magnet Weight	0.64 kg	QES	0.30
Total Weight	2.17 kg	QTS	0.28
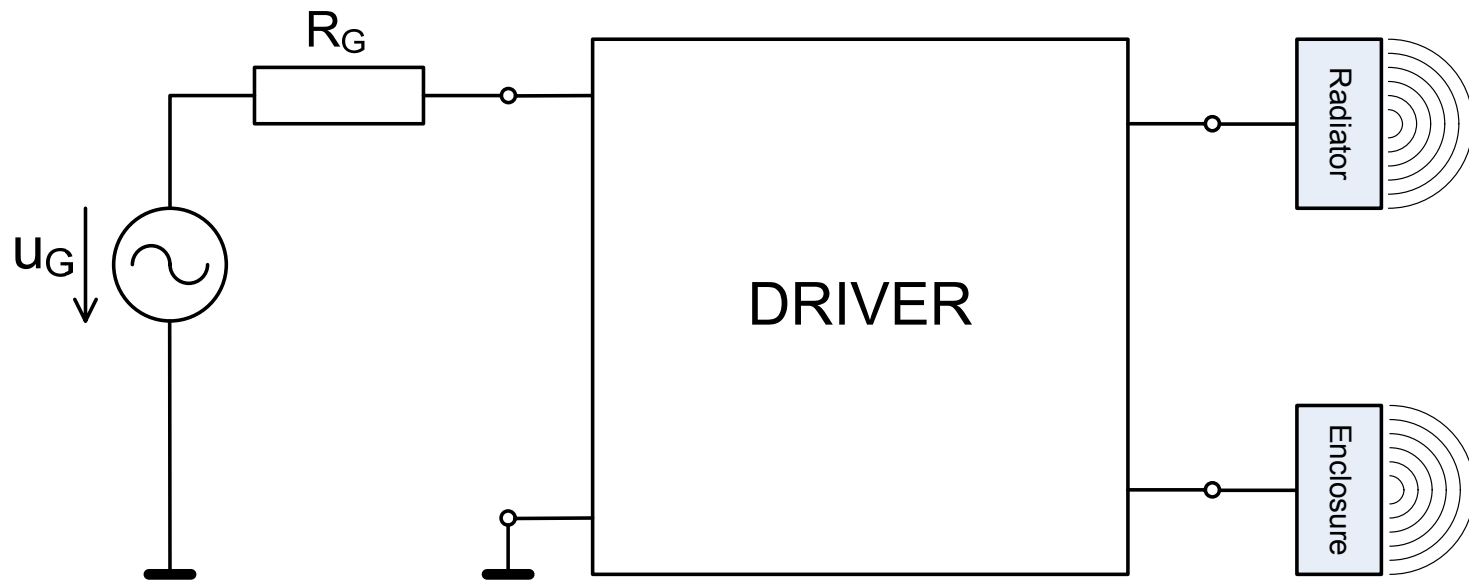
# Nízkotónový reproduktor v basreflexovej ozvučnici (Driver, Radiator, Enclosure)



- $\alpha=3.65, h=1.35, q=1.7$
- $D_{p,min}=10\text{cm}$

# Skript nízkotónovej časti

| Seas Prestige CA26RE4X H1316  
|  $R_{vc}=6.1\Omega$ ;  $L_{vc}=3.08\text{mH}$ ;  $B_l=11.6\text{N/A}$ ;  $M_{md}=38.5\text{g}$ ;  
|  $M_{mrd}=3.8\text{g}$ ;  $R_{ms}=1.66\text{Ns/m}$ ;  $C_{ms}=1.1\text{mm/N}$ ;  $S_d=350\text{cm}^2$   
|  $f_s=25\text{Hz}$ ;  $Q_{ts}=0.28$ ;  $Q_{ms}=3.99$ ;  $Q_{es}=0.30$ ;  $V_{as}=164\text{lit}$ ;  
|  $y_{max}=4\text{mm}$ ;  $sens=91\text{dB}$ ;  $P_{e(lt)}=80\text{W}$

Def\_Driver 'Woofers'


$S_D=350\text{cm}^2$   $d_{D1}=5.5\text{cm}$   $t_{D1}=6.5\text{cm}$  |Cone  
 $f_s=25\text{Hz}$   $V_{as}=164\text{L}$   $Q_{ms}=3.99$   
 $Q_{es}=0.3$   $R_e=6.1\Omega$   $L_e=3.08\text{mH}$   $\text{Expo}L_e=0.618$

System 'L'

Driver 'D1' Def='Woofers' Node=1=0=2=3  
Radiator 'Rad1' Def='D1' Node=2  
 $x=0$   $y=0$   $z=0$   $H\text{Angle}=0$   $V\text{Angle}=0$   
Enclosure 'E1' Node=3  
 $V_b=45\text{L}$   $S_b=350\text{cm}^2$   
 $f_b=34\text{Hz}$   $d_D=10\text{cm}$   $Q_D/f_0=0.34$   $\text{Visc}=0$   
 $x=0$   $y=0$   $z=0$   $H\text{Angle}=0$   $V\text{Angle}=0$


# Hladina akustického tlaku

## 7. Sound Pressure of L10, Lp (Phase)

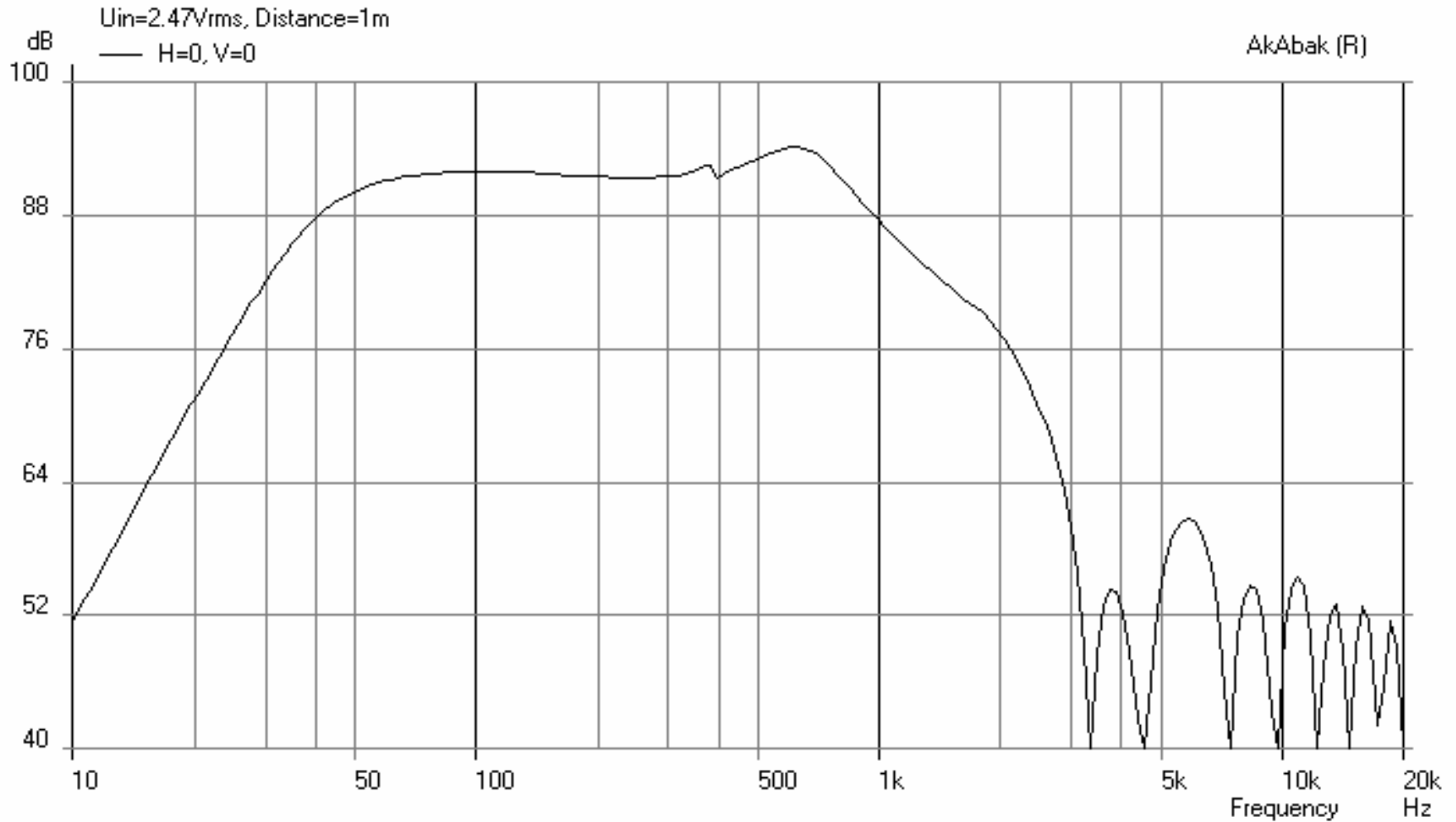

# Stredotónový reproduktor


- QTC=0.9; a=1.58;

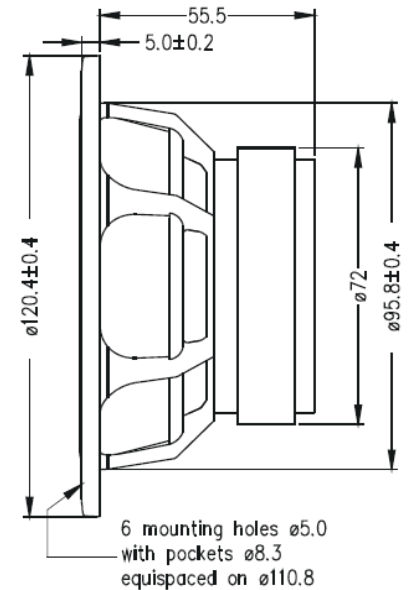

Nominal Impedance	8 Ohms	Voice Coil Resistance	6.3 Ohms
Recommended Frequency Range	400 - 5000 Hz	Voice Coil Inductance	0.31 mH
Short Term Power Handling *	400 W	Force Factor	4.2 N/A
Long Term Power Handling *	110 W	Free Air Resonance	68 Hz
Characteristic Sensitivity (2.83V, 1m)	86.0 dB	Moving Mass	4.58 g
Voice Coil Diameter	26 mm	Air Load Mass In IEC Baffle	0.24 g
Voice Coil Height	5.8 mm	Suspension Compliance	1.2 mm/N
Air Gap Height	4.0 mm	Suspension Mechanical Resistance	0.85 Ns/m
Linear Coil Travel (p-p)	1.8 mm	Effective Piston Area	55 cm <sup>2</sup>
Maximum Coil Travel (p-p)	-	VAS	5 Litres
Magnetic Gap Flux Density	1.1 T	QMS	2.42
Magnet Weight	0.25 kg	QES	0.74
Total Weight	0.66 kg	QTS	0.56

# Stredotónový reproduktor v zatvorenej ozvučnici

(Driver, Radiator, Enclosure)

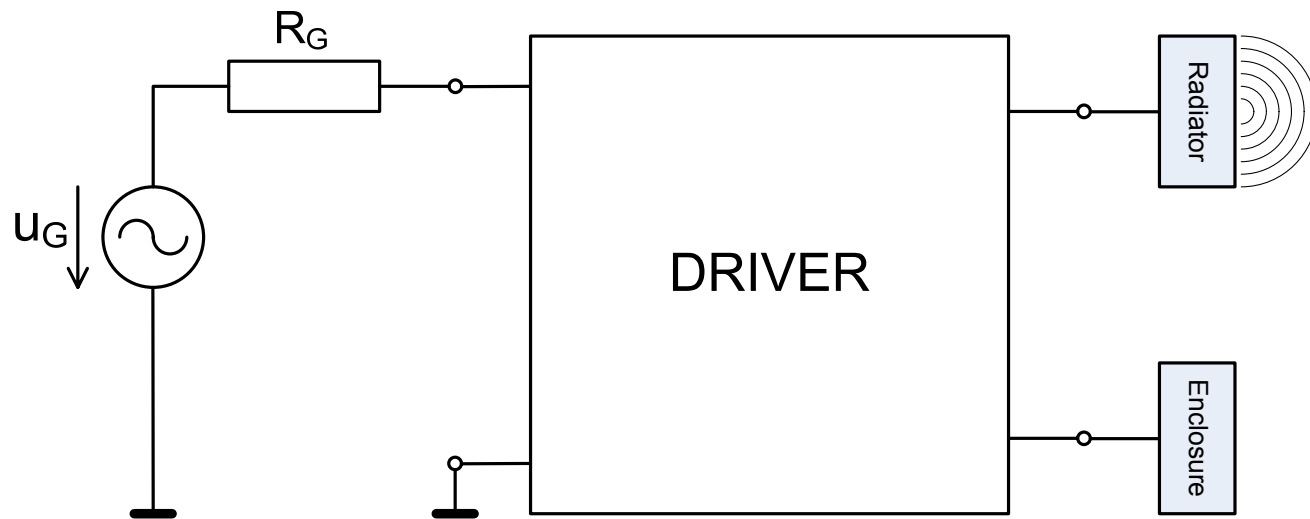

- $QTC=0.9$ ;  $a=1.58$ ;

# Skript stredotónovej časti

| Seas Prestige MCA12RC H1304  
| Revc=6.3Ohms; Levc=0.31mH; Bl=4.2N/A; Mmd=4.58g;  
|Mmrd=0.24g; Rms=0.85Ns/m; Cms=1.2mm/N;  
|Sd=55cm<sup>2</sup>; Fs=68Hz; Qts=0.56; Qms=2.42; Qes=0.74; Vas=5lit.;  
|ymax=0.9mm; sens=86dB; Pe(lt)=110W

Def\_Driver 'Midrange'

SD=55cm<sup>2</sup> dD1=3.6cm tD1=2.75cm |Cone  
fs=68Hz Vas=5L Qms=2.42  
Qes=0.74 Re=6.2ohm Le=0.31mH ExpoLe=0.618

System 'M'

Driver 'D2' Def='Midrange' Node=1=0=4=5

Radiator 'Rad1' Def='D2' Node=4

x=0 y=0 z=0 HAngle=0 VAngle=0

Enclosure 'E2' Node=5

Vb=1.75L Sb=55cm<sup>2</sup>




# Hladina akustického tlaku stredotónovej časti

17. Sound Pressure of L10, Lp (Phase)


$U_{in}=2.49V_{rms}$ , Distance=1m

—  $H=0, V=0$

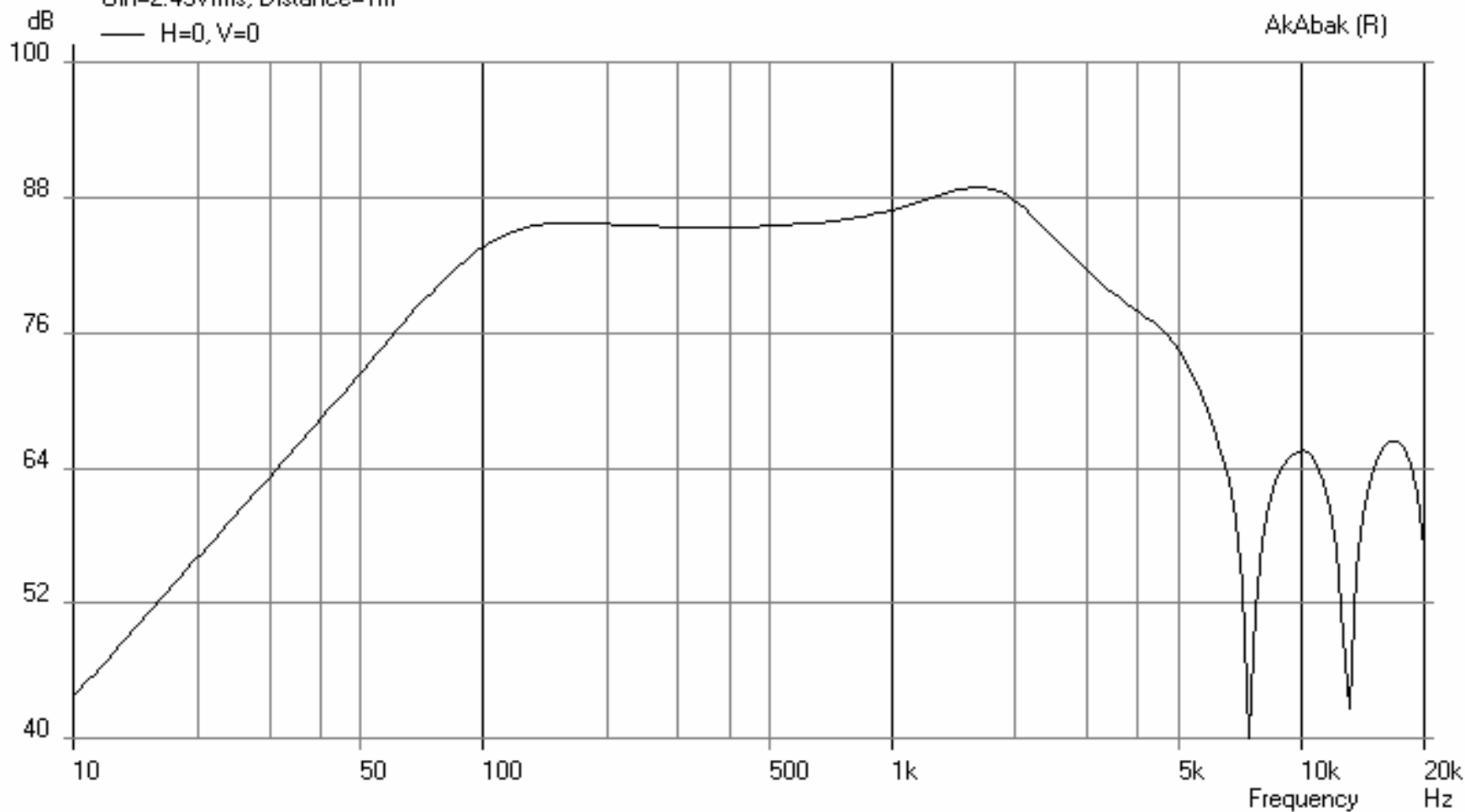

# Vysokotónový reproduktor


• ...

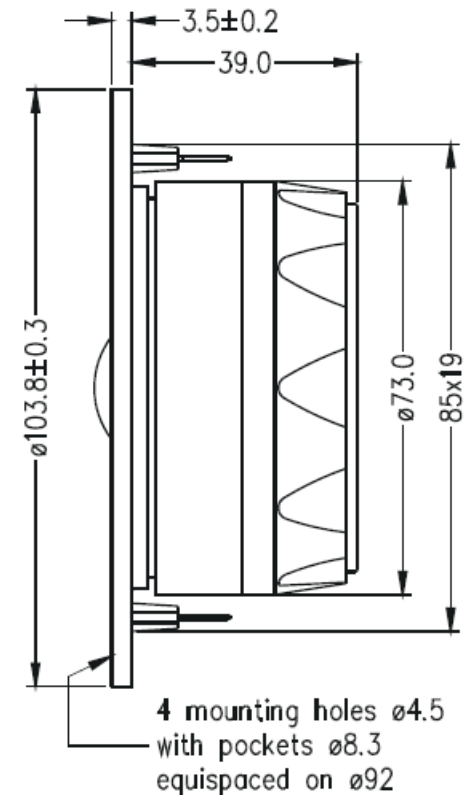

Nominal Impedance	6 Ohms	Voice Coil Resistance	4.8 Ohms
Recommended Frequency Range	1500 - 25000 Hz	Voice Coil Inductance	0.05 mH
Short Term Power Handling *	220 W	Force Factor	3.5 N/A
Long Term Power Handling *	90 W	Free Air Resonance	550 Hz
Characteristic Sensitivity (2.83V, 1m)	90 dB	Moving Mass	0.37 g
Voice Coil Diameter	26 mm	Effective Piston Area	7.5 cm <sup>2</sup>
Voice Coil Height	1.5 mm	Magnetic Gap Flux Density	1.8 T
Air Gap Height	2.0 mm	Magnet Weight	0.25 kg
Linear Coil Travel (p-p)	0.5 mm	Total Weight	0.50 kg

# Vysokotónový reproduktor (Speaker)

• ...

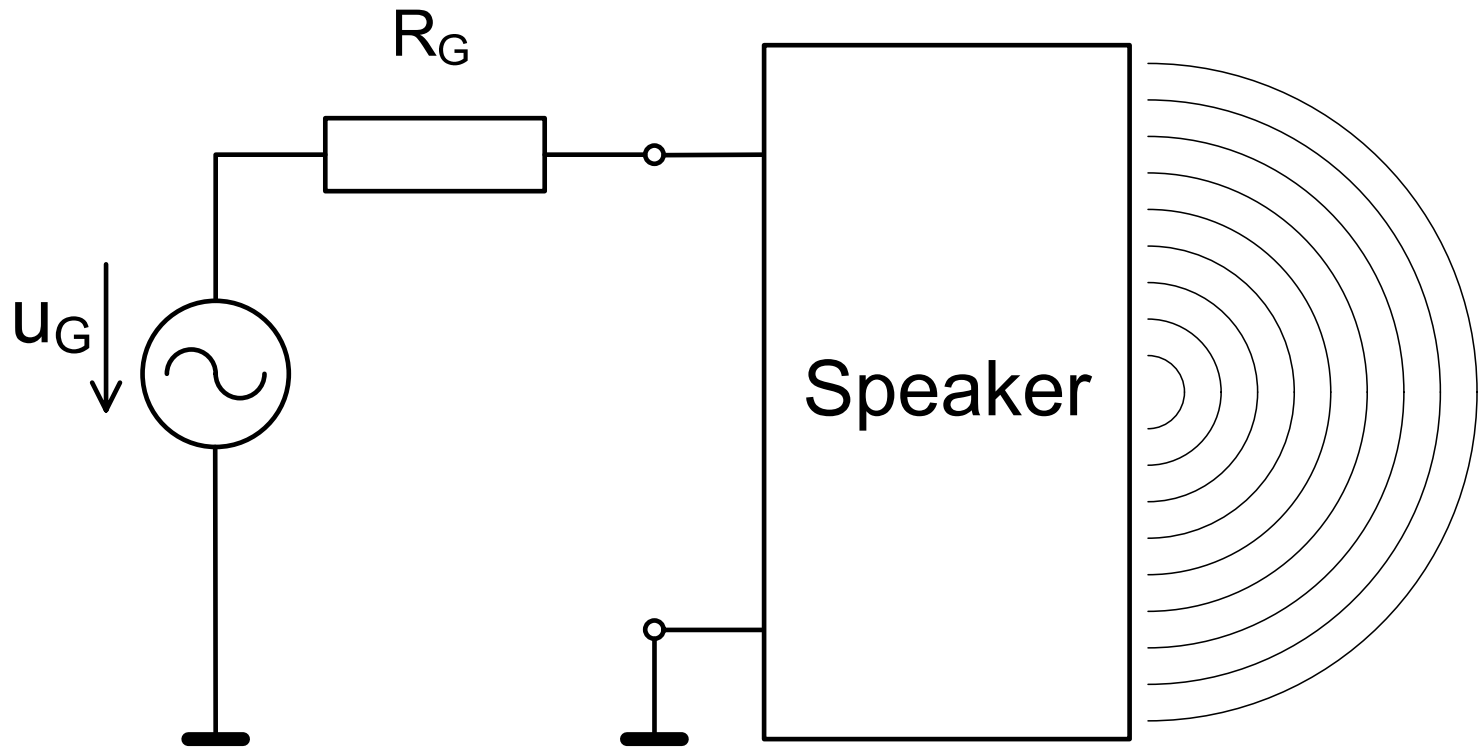

# Skript vysokotónovej časti

| Seas Prestige 27TDFC H1189

|  $R_{vc}=4.8\Omega$ ;  $L_{vc}=0.05\text{mH}$ ;  $Bl=3.5\text{N/A}$ ;  $M_{ms}=0.37\text{g}$ ;  $S_d=7.5\text{cm}^2$

|  $f_s=550\text{Hz}$ ;  $y_{max}=0.25\text{mm}$ ;  $sens=90\text{dB}$ ;  $P_e(1t)=90\text{W}$

Def\_Speaker 'Tweeter'

Meas\_Dipole

$SD=7.5\text{cm}^2$   $tD1=5.5\text{mm}$   $t1=3.5\text{mm}$  |Convex Dome

$f_s=550\text{Hz}$   $V_{as}=17.8\text{cm}^3$   $Q_{ms}=2.425$

$Bl=3.5\text{Tm}$   $R_e=4.8\Omega$   $L_e=50\mu\text{H}$   $\text{Expo}L_e=0.618$

System 'T'

Speaker 'Sp1' Def='Tweeter' Node=1=0


$x=0$   $y=0$   $z=0$   $H\text{Angle}=0$   $V\text{Angle}=0$

# Hladina akustického tlaku


25. Sound Pressure of L10, Lp (Phase)


$U_{in}=2.2V_{rms}$ , Distance=1m

— H=0, V=0

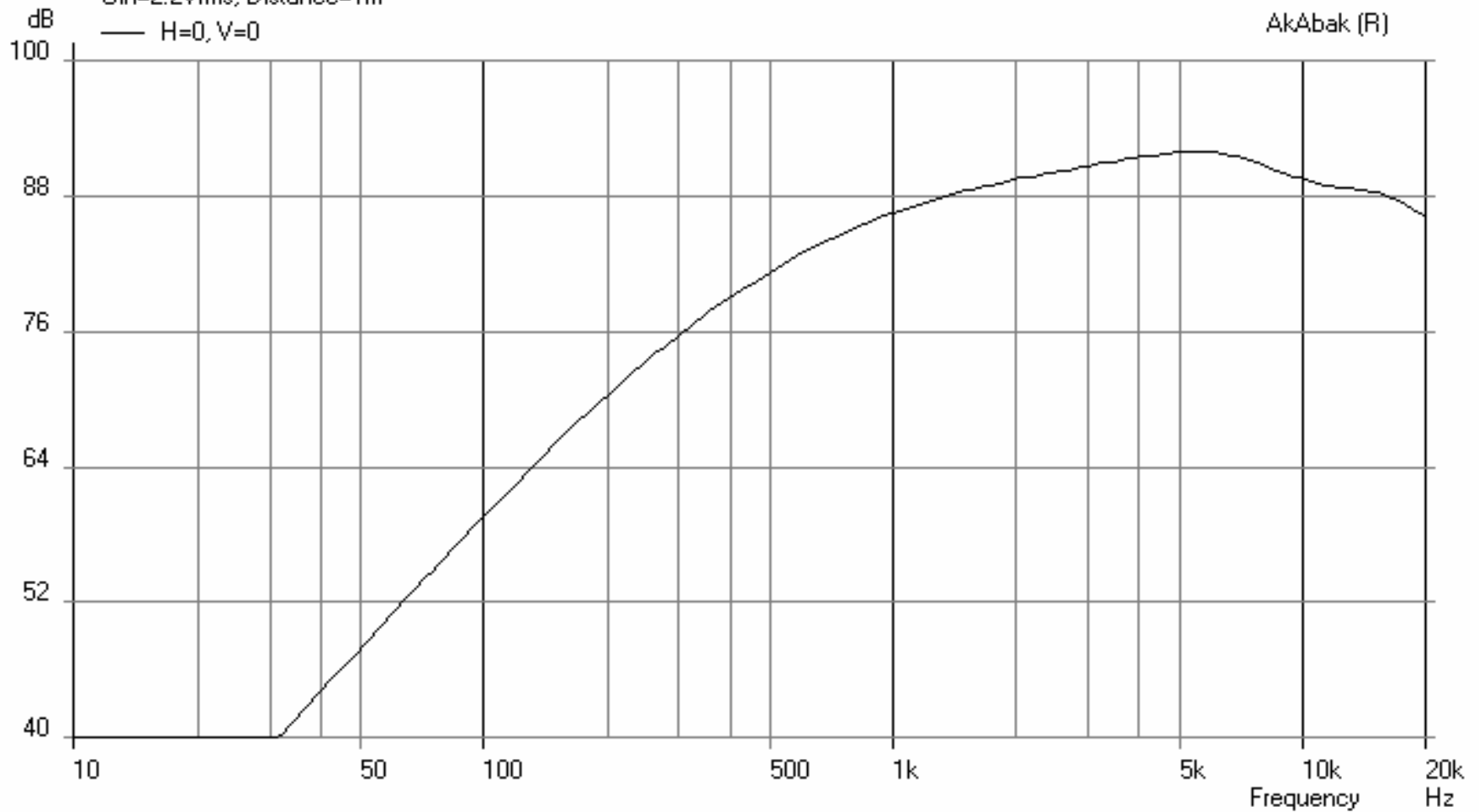
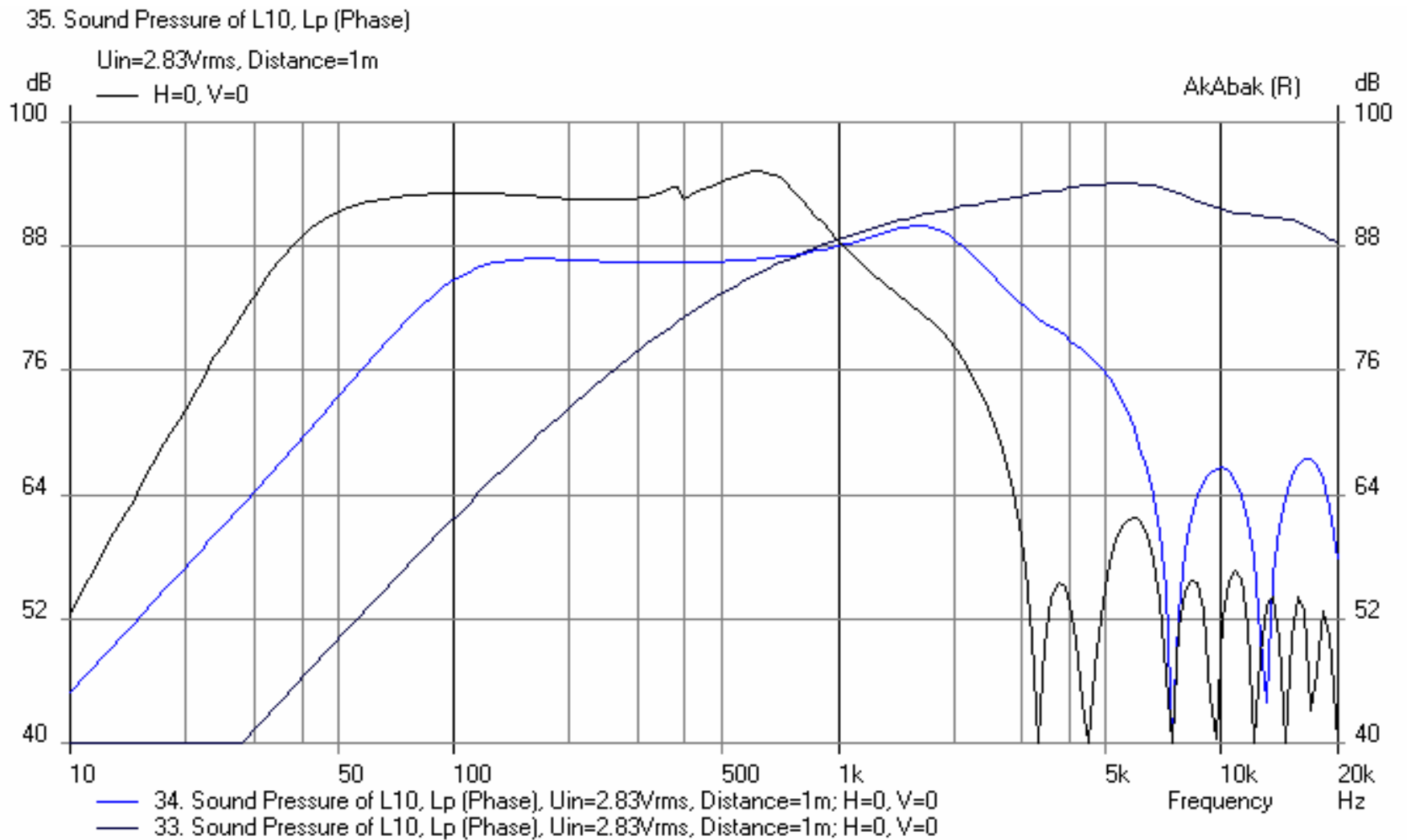
# Hladiny akustických tlakov v troch subpásmach - porovnanie



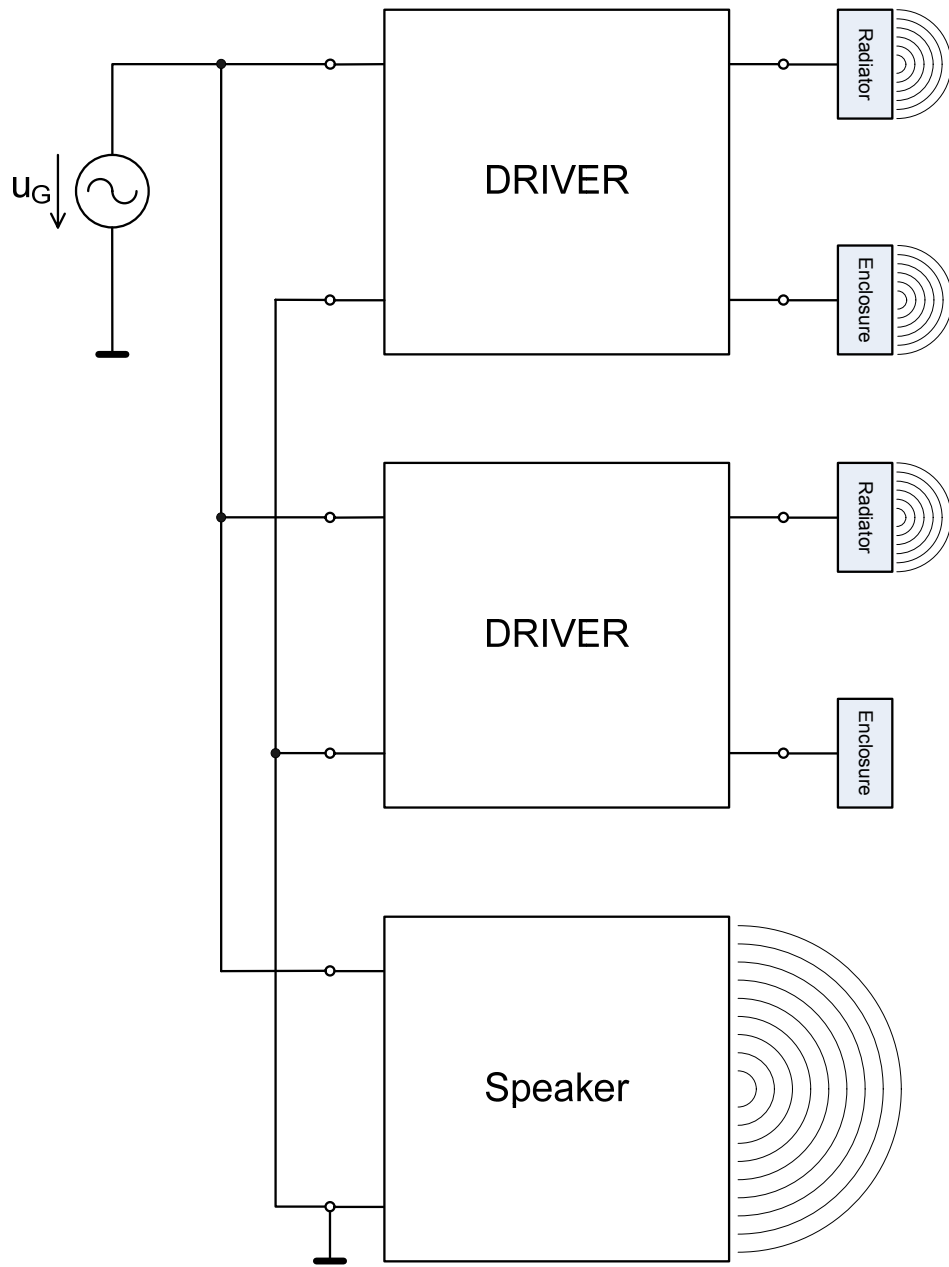

Všetky tri  
reproduktory  
dohromady

## Def\_Driver 'Woofers'

SD=350cm<sup>2</sup> dD1=5.5cm tD1=6.5cm |Cone  
fs=25Hz Vas=164L Qms=3.99 Qes=0.3 Re=6.1ohm Le=3.08mH ExpoLe=0.618

## Def\_Driver 'Midrange'

SD=55cm<sup>2</sup> dD1=3.6cm tD1=2.15cm |Cone  
fs=68Hz Vas=5L Qms=2.42 Qes=0.74 Re=6.2ohm Le=0.31mH ExpoLe=0.618

## Def\_Speaker 'Tweeter'

### Meas\_Dipole

SD=7.5cm<sup>2</sup> tD1=5.5mm t1=3.5mm |Convex Dome  
fs=550Hz Vas=17.8cm<sup>3</sup> Qms=2.425 Bl=3.5Tm Re=4.8ohm Le=50uH ExpoLe=0.618

## System 'L'

Driver 'D1' Def='Woofers' Node=1=0=2=3

Radiator 'Rad1' Def='D1' Node=2

x=0 y=0 z=0 HAngle=0 VAngle=0

Enclosure 'E1' Node=3

Vb=45L Sb=350cm<sup>2</sup> fb=34Hz dD=10cm QD/fo=0.34 Visc=0

x=0 y=0 z=0 HAngle=0 VAngle=0

## System 'M'

Driver 'D2' Def='Midrange' Node=1=0=4=5

Radiator 'Rad1' Def='D2' Node=4

x=0 y=0 z=0 HAngle=0 VAngle=0

Enclosure 'E2' Node=5

Vb=3.2L Sb=55cm<sup>2</sup>

## System 'T'

Speaker 'Sp1' Def='Tweeter' Node=1=0

x=0 y=0 z=0 HAngle=0 VAngle=0




# Celková hladina akustického tlaku pri rovnakej polarite reproduktorov


37. Sound Pressure of L10, Lp (Phase)

Uin=2.83Vrms, Distance=1m


— H=0, V=0

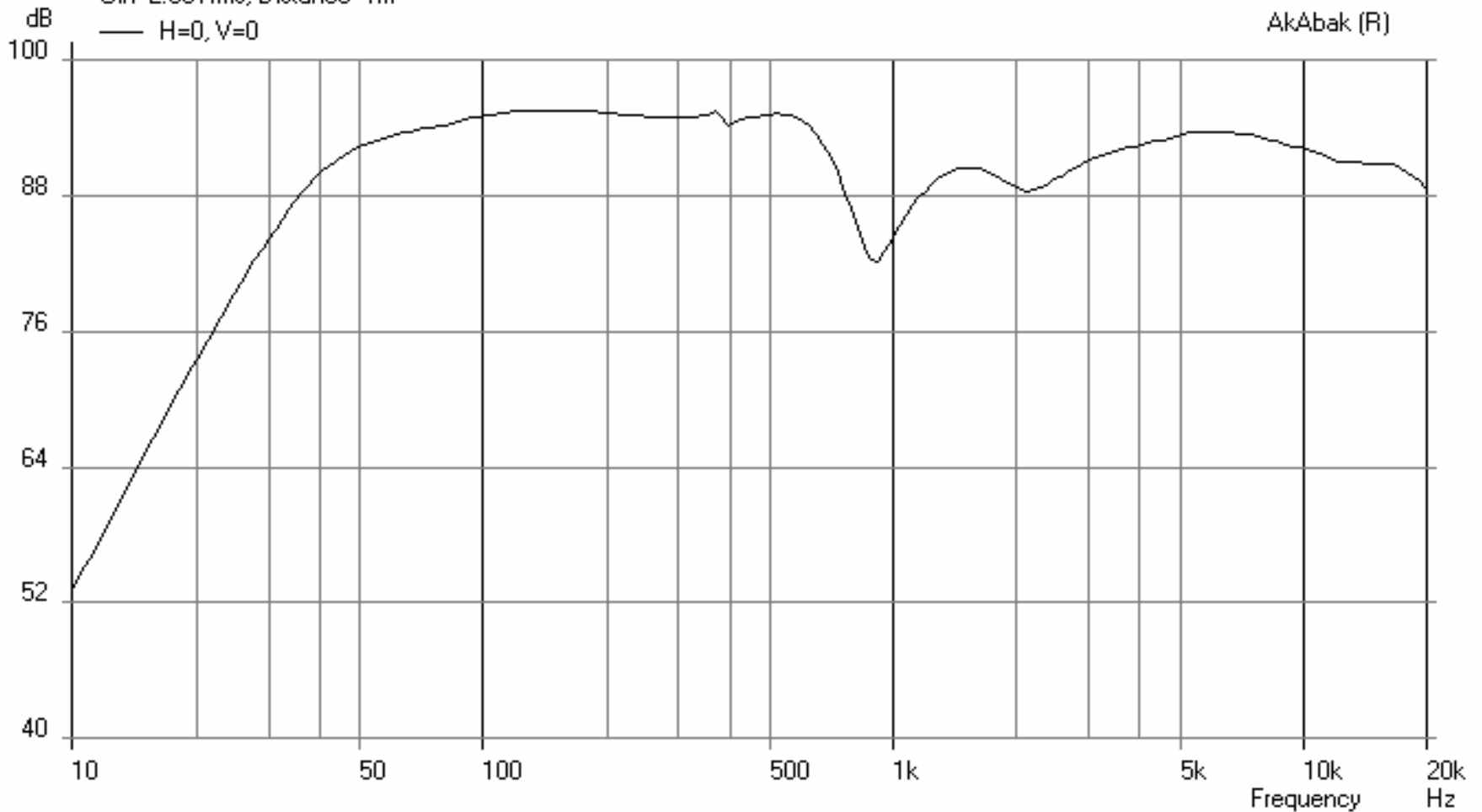
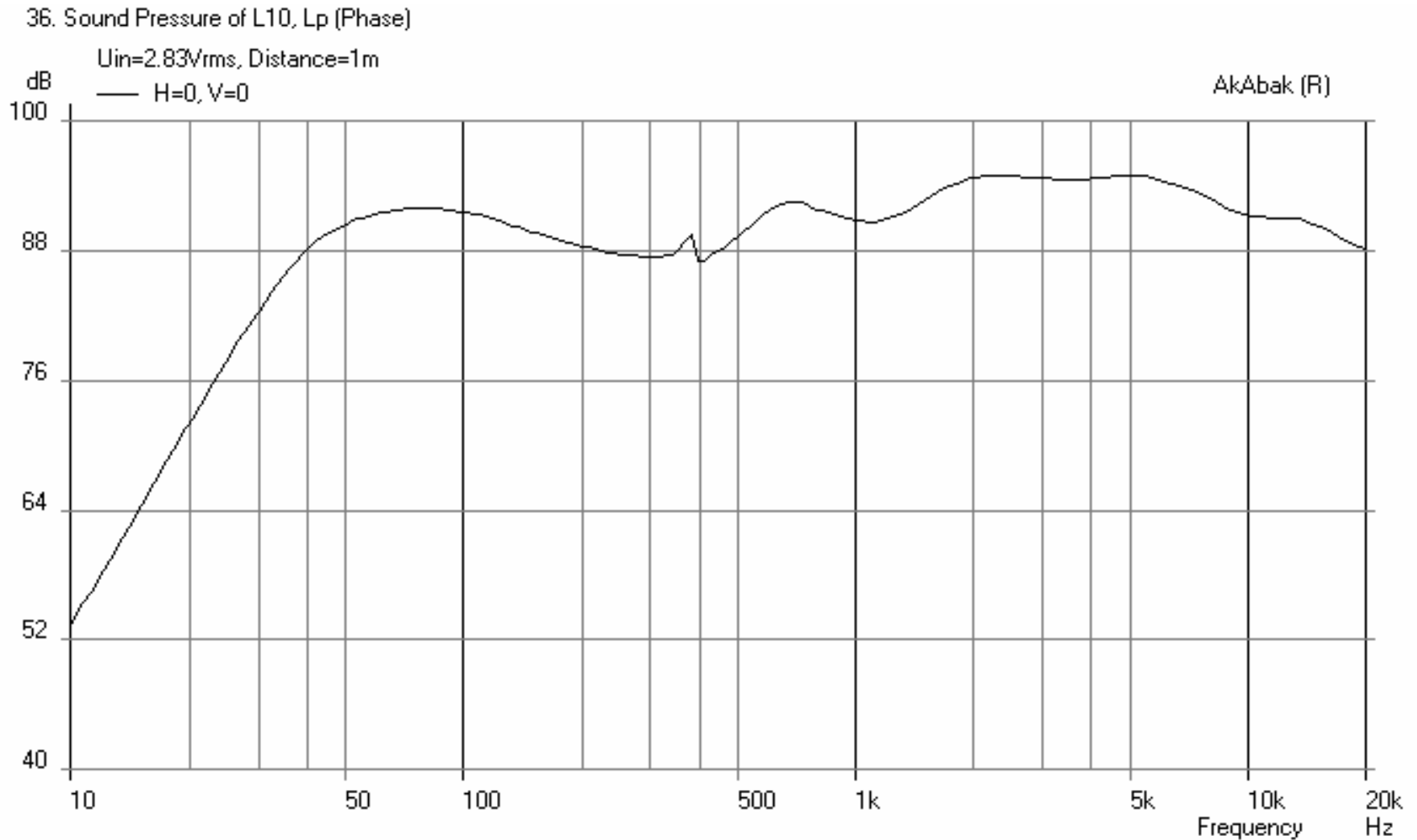
# Celková hladina akustického tlaku: opačná polarita stredotónového reproduktora


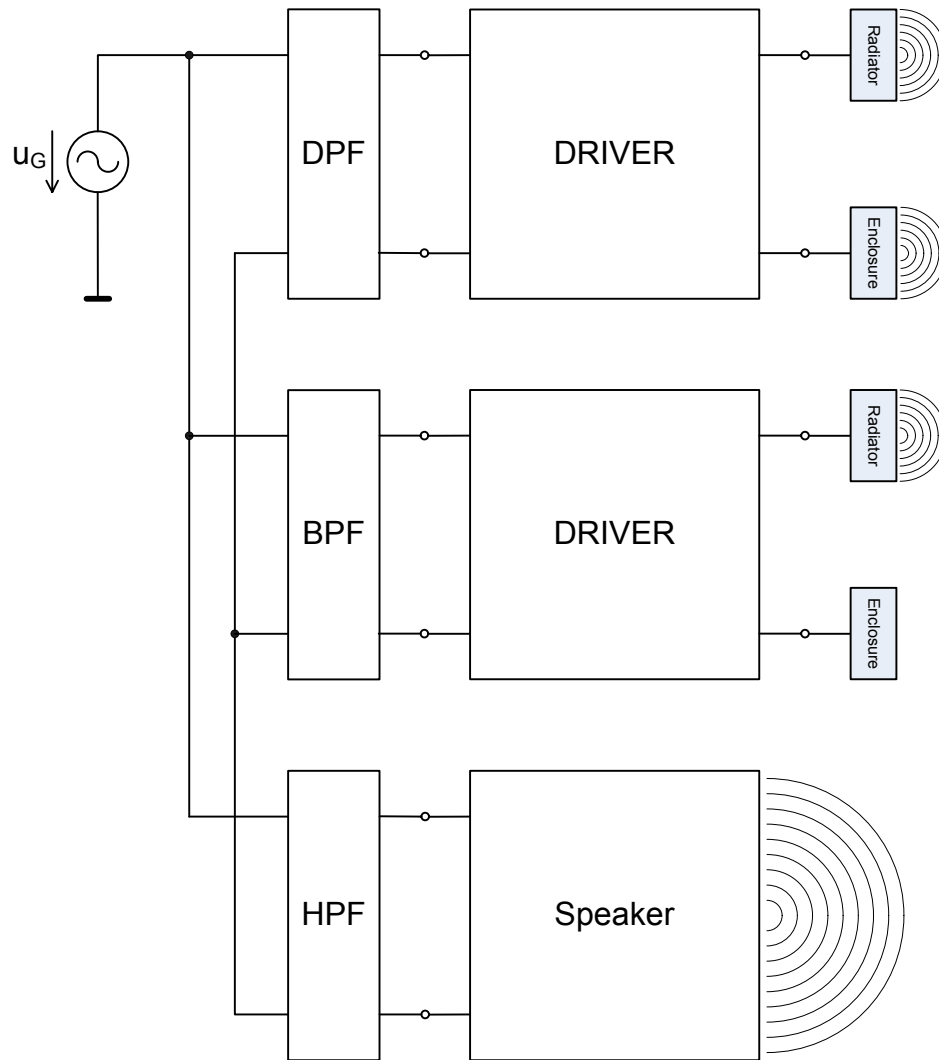
# Použitie elektrických filtrov vo funkcii „výhybiiek“



# Filter-Dialog: Dolnopriepustný filter

(Butterworth, 2. rád)

$$H(s) = \frac{1}{s_0^2 + 1.414214s_0 + 1} \quad s_0 = \frac{s}{\omega_0}$$

1. Standard Lowpass Functions
2. Výber „Order“ a „Class“ filtra
3. Copy to 1
4. Vloženie „Filter identif.“, „Filter frequency f0“ a „Amplification“
5. Copy function 1 to clipboard and close

**Filter**

Transfer 1

Get from script

Copy to 2

Clear 1

Copy function 1 to clipboard and close

Filter identif.  Filter frequency fo  ..Hz.. Amplification yo   Diagram

```
b0=1;
a2=1; a1=1.414214; a0=1;
```

Transfer 2

+1

$1*s^2 + 1.414*s + 1$

Standard lowpass functions...  Lowpass to highpass  Highpass to lowpass  Lowpass to allpass

Bessel allpass delay...  Lowpass to bandpass Bandwidth:  f1  f2  ..Hz..

Copy to 1  Deci  Frequency scaling  Factor  To level  dB

Clear 2

**Standard Lowpass Functions**

Order

Class

Butterworth

Bessel

Linkwitz-Riley

Chebyshev Ripple  dB

Bu-LR Compromise Ripple  dB

Bu-Thomson M


# AFCH dolnopriepustného filtra

(Butterworthov filter 2. rádu)

31. Voltage of L10, Level (Phase)

$U_{in}=2.83V_{rms}$

dB — L, N=1=0, U1

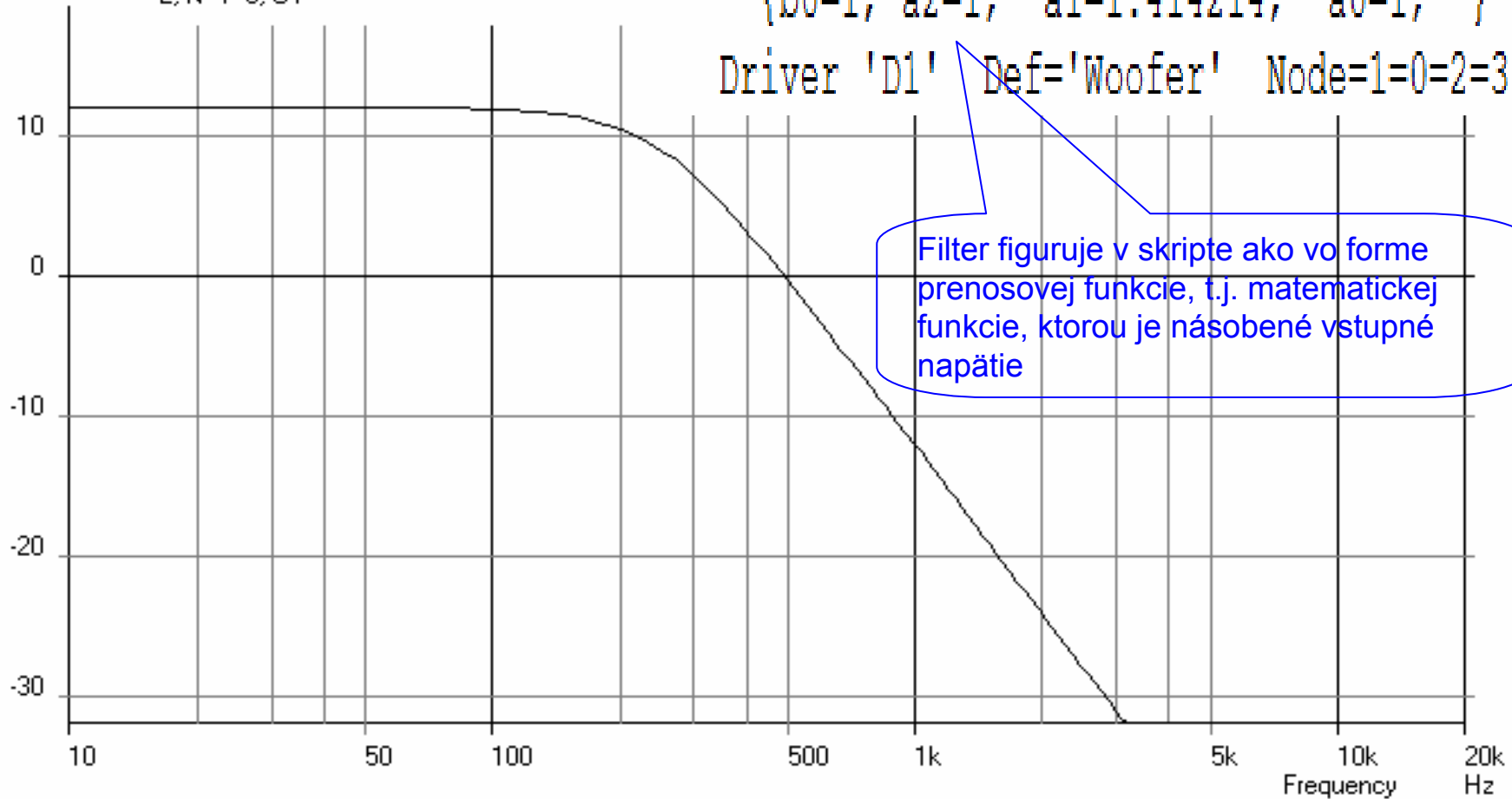

System 'L'

Filter 'LPF-B'


$f_o=250Hz$   $v_o=1$

$\{b_0=1; a_2=1; a_1=1.414214; a_0=1; \}$

Driver 'D1' Def='Woofer' Node=1=0=2=3

Filter figuruje v skripte ako vo forme prenosovej funkcie, t.j. matematickej funkcie, ktorou je násobené vstupné napätie
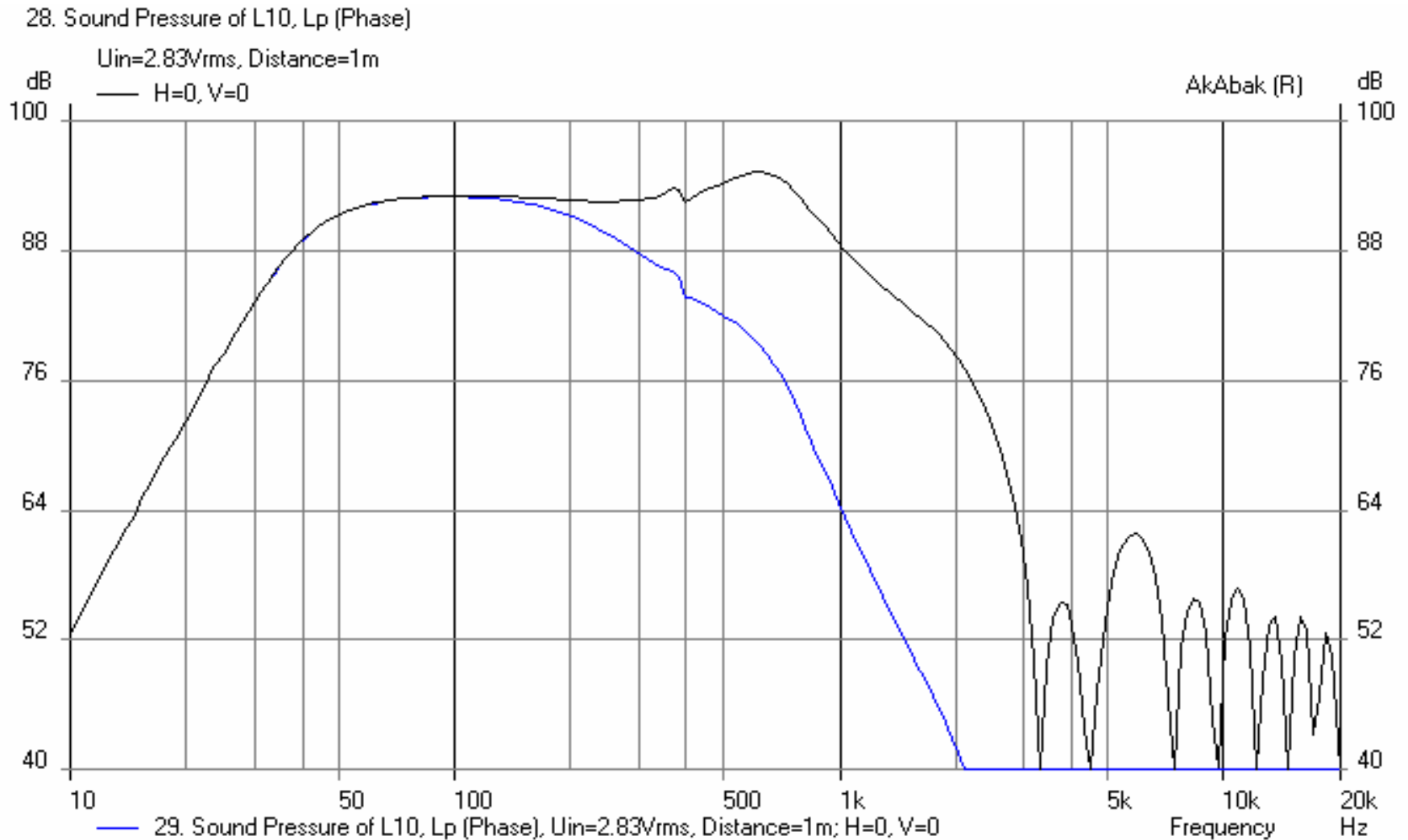
# Hladina akustického tlaku nízkotónovej časti pred filtráciou a po filtrácii



# Filter-Dialog: Pásmový priepust (Butterworth, 4. rád)

$$H(s) = \frac{s_0^2}{0.163s_0^4 + 0.571s_0^3 + 1.327s_0^2 + 0.571s_0 + 1} \quad s_0 = \frac{s}{\omega_0}$$

**Filter**

Transfer 1

Filter identif.	Filter frequency fo	Amplification yo
BPF-B	707.107Hz	1

b2=1;  
a4=0.163265; a3=0.571429; a2=1.326531;  
a1=0.571429; a0=0.163265;

Transfer 2

1\*s<sup>2</sup>

0.163\*s<sup>4</sup> + 0.571\*s<sup>3</sup> + 1.327\*s<sup>2</sup> + 0.571\*s + 0.163

Standard lowpass functions...    Lowpass to highpass    Highpass to lowpass    Lowpass to allpass

Bessel allpass delay...    Lowpass to bandpass    Bandwidth: 250    f1: 250    f2: 2000

Copy to 1    Deci    Frequency scaling    Factor    To level    -3dB    dB

Clear 2

1. Standard Lowpass Functions
2. Výber „Order“ a „Class“ filtra
3. Vložit „Bandwith“ – frekvencie f1 a f2 (požadované medzné frekvencie pásmového priepustu)
4. Lowpass to bandpass
5. Copy to 1
6. Vloženie „Filter identif.“ a „Amplification“ (filter frequency f0 je automaticky vypočítaná ako geometrický priemer frekvencií f1 a f2)
7. Copy function 1 to clipboard and close

# AFCH pásmového priepustu (Butterworthov, 2. rád)

34. Voltage of L10, Level (Phase)

$U_{in}=2.83V_{rms}$

dB — M, N=1=0, U1

System 'M'


Filter 'BPF-B'

$f_o=707.107Hz$   $v_o=1$

```
{b2=1; a4=0.163265; a3=0.571429; a2=1.326531;  
a1=0.571429; a0=0.163265; }
```


Driver 'D2' Def='Midrange' Node=1=0=4=5

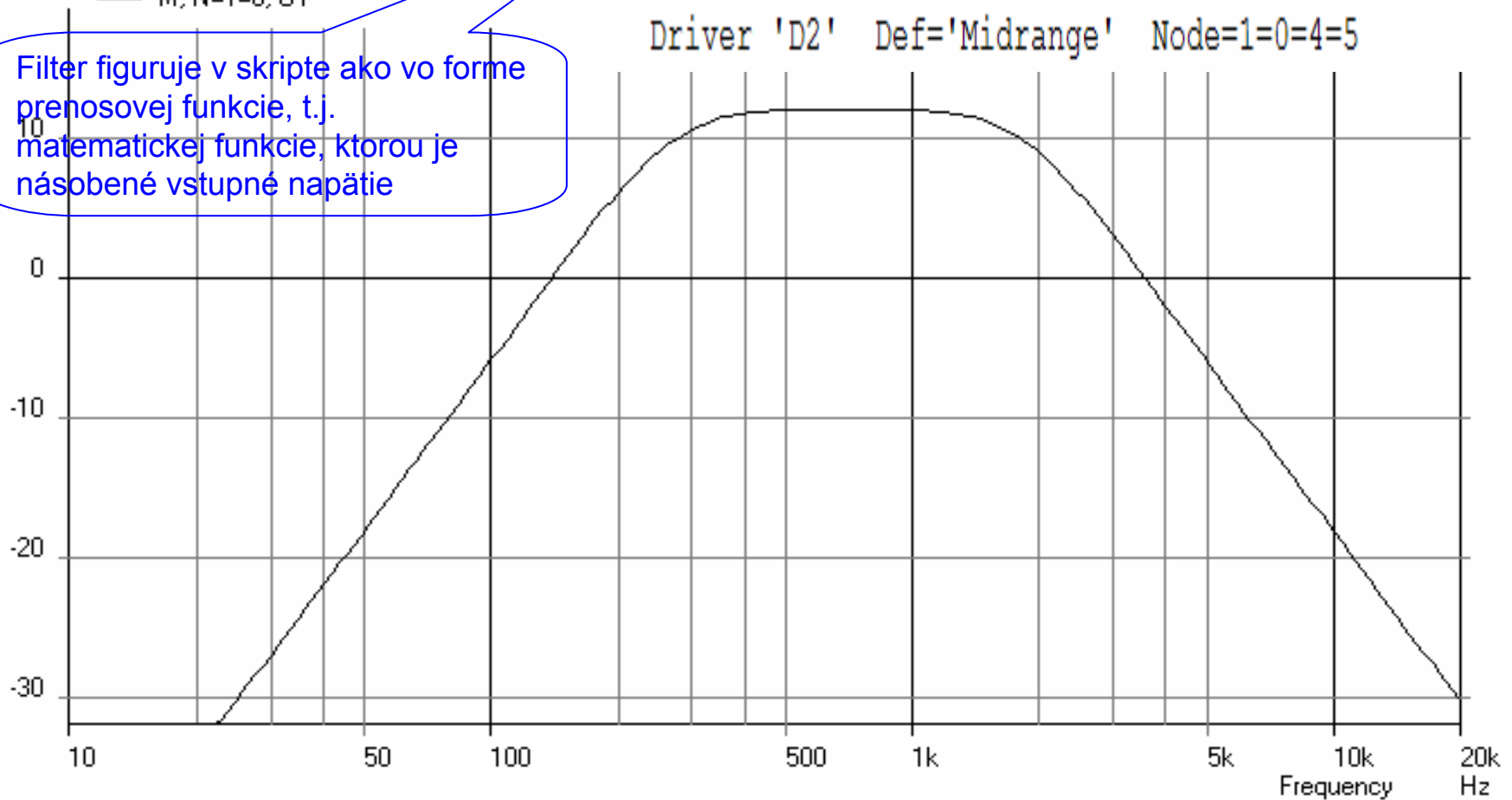Filter figuruje v skripte ako vo forme  
prenosovej funkcie, t.j.  
matematickej funkcie, ktorou je  
násobené vstupné napätie




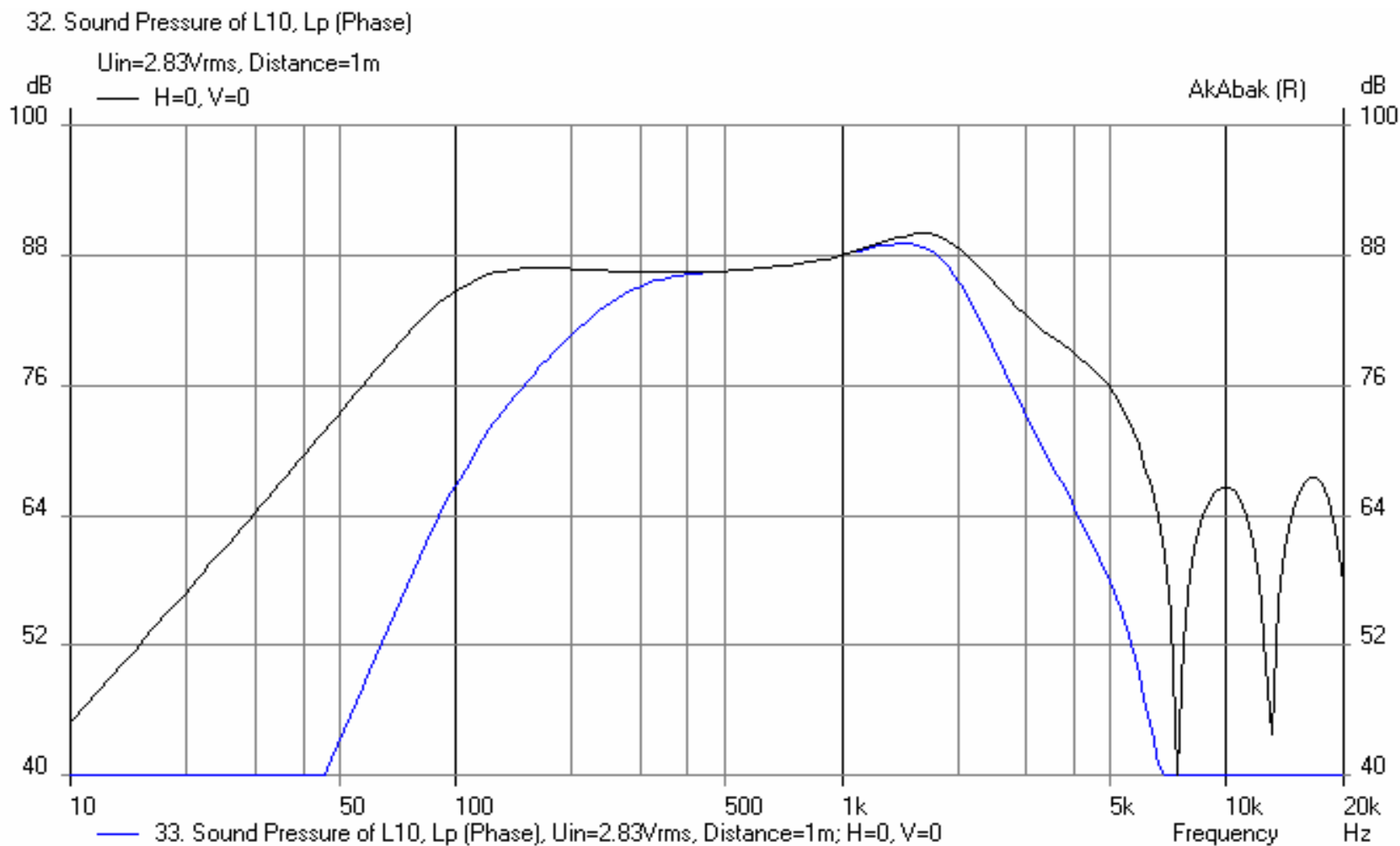
# Hladina akustického tlaku stredotónovej časti pred filtráciou a po filtrácii



Filter-Dialog: Hornopriepustný  
filter  
(Butterworth, 2. rád)

$$H(s) = \frac{s_0^2}{s_0^2 + 1.414s_0 + 1} \quad s_0 = \frac{s}{\omega_0}$$

The screenshot shows a 'Filter' dialog box with the following fields and options:

- Transfer 1:**
  - Get from script
  - Copy to 2
  - Clear 1
  - Copy function 1 to clipboard and close
- Filter parameters:**
  - Filter identif.: HPF-B2
  - Filter frequency fo: 2000 Hz
  - Amplification yo: 1
  - Diagram
- Transfer 2:**
  - 1\*s^2
  - 1\*s^2 + 1.414\*s + 1
- Filter type selection:**
  - Standard lowpass functions...
  - Lowpass to highpass
  - Highpass to lowpass
  - Lowpass to allpass
  - Bessel allpass delay...
  - Lowpass to bandpass
  - Bandwidth: f1, f2 ..Hz..
  - Copy to 1
  - Deci
  - Clear 2
  - Frequency scaling
  - Factor:  To level:  -3dB dB

1. Standard Lowpass Functions
2. Výber „Order“ a „Class“ filtra
3. Lowpass to highpass
4. Copy to 1
5. Vloženie „Filter identif.“, „Filter frequency f0“ a „Amplification“
6. Copy function 1 to clipboard and close

# AFCH hornopriepustného filtra (Butterworthov, 2. rád)

System 'T'

Filter 'HPF-B2'

fo=2kHz vo=1

```
{b2=1; a2=1; a1=1.414214; a0=1; }
```


Speaker 'Sp1' Def='Tweeter' Node=1=0

x=0 y=0 z=0 HAngle=0 VAngle=0

4. Voltage of L10, Level (Phase)


Uin=2.83Vrms

dB — T, N=1=0, U1

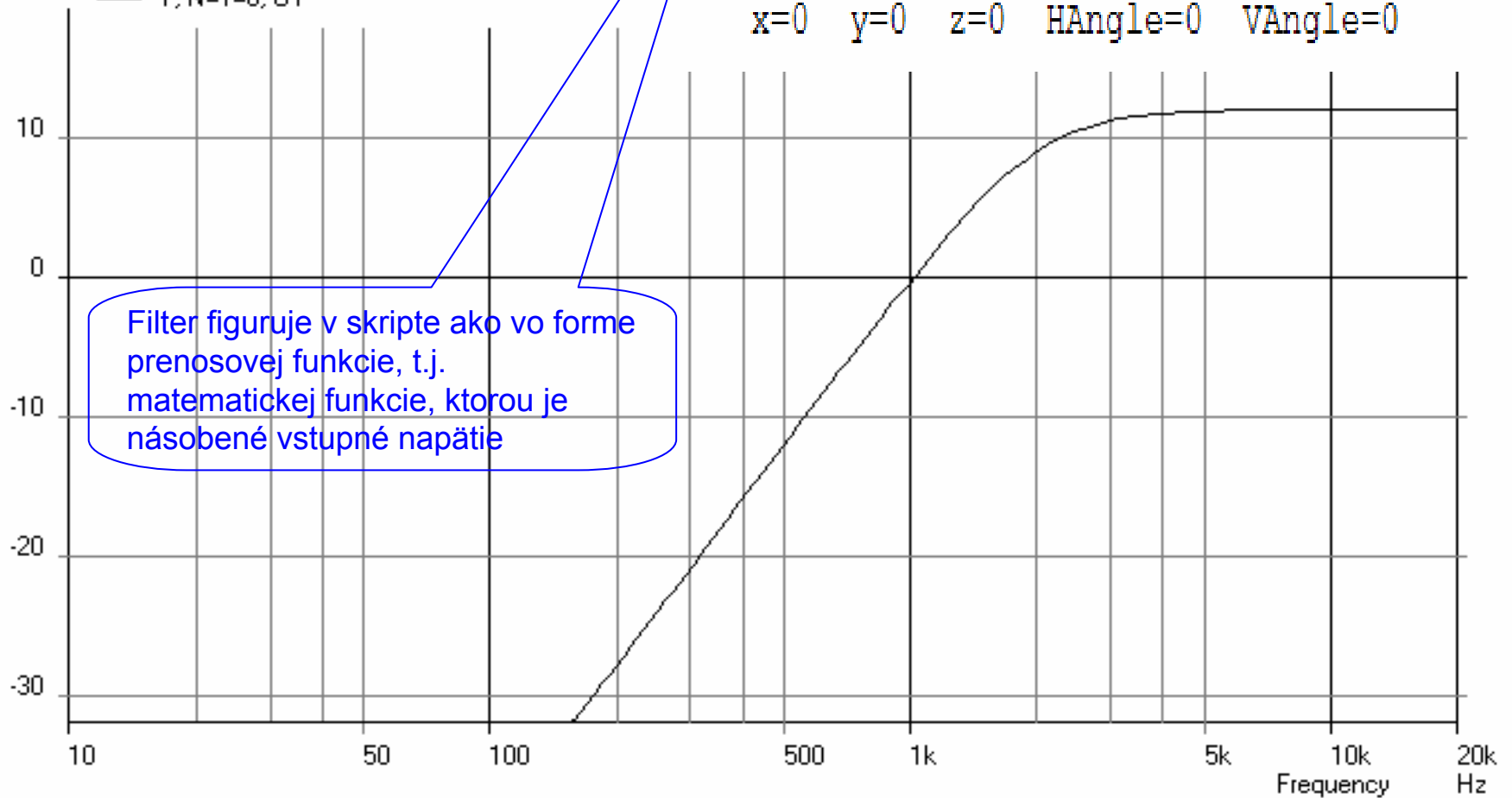


Filter figuruje v skripte ako vo forme prenosovej funkcie, t.j. matematickej funkcie, ktorou je násobené vstupné napätie
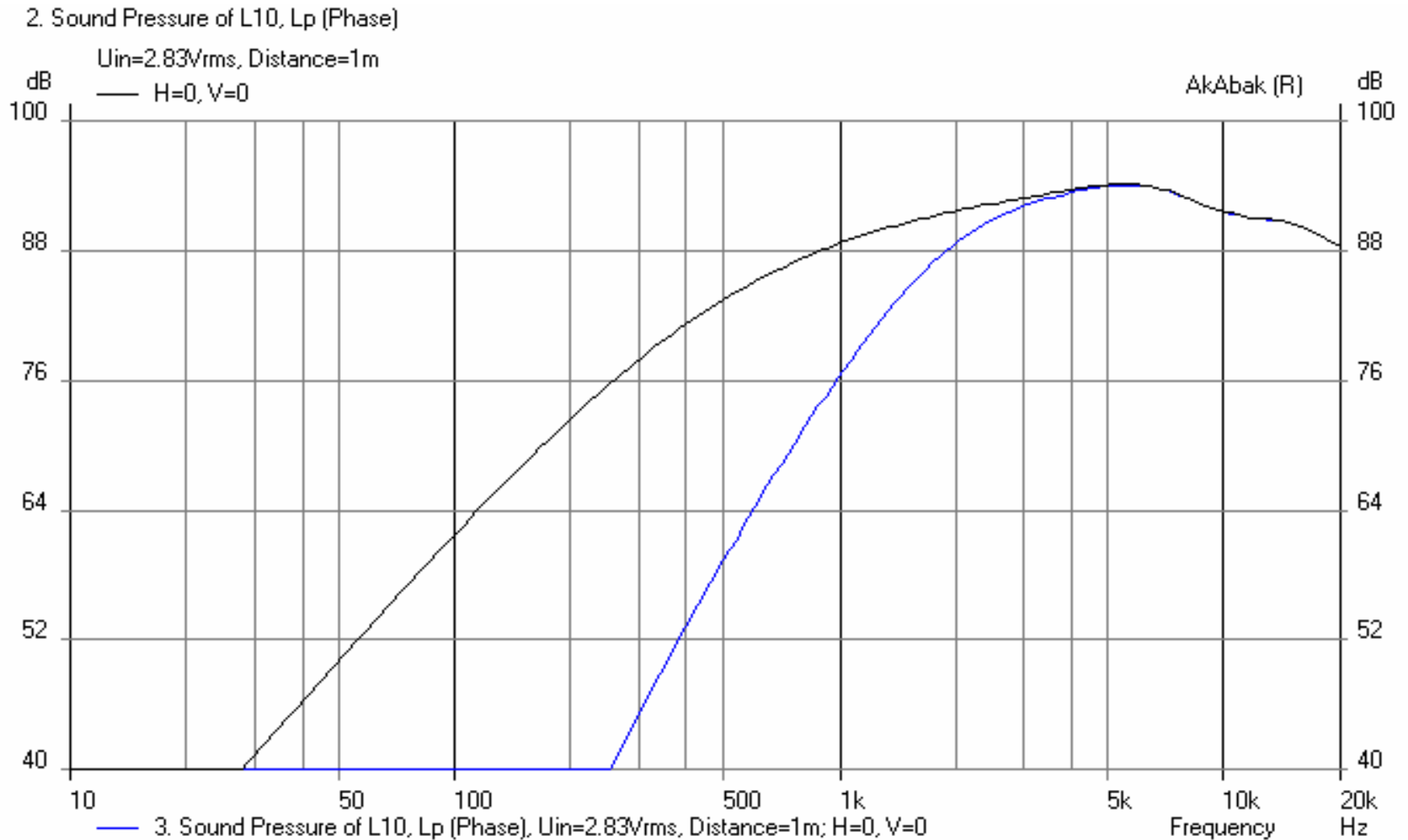
# Hladina akustického tlaku vysokotónovej časti pred filtráciou a po filtrácii




# AFCH dolnopriepustného filtra, pásmového priepustu a hornopriepustného filtra: porovnanie (Butterworth, 2. rád)

6. Voltage of L10, Level (Phase)

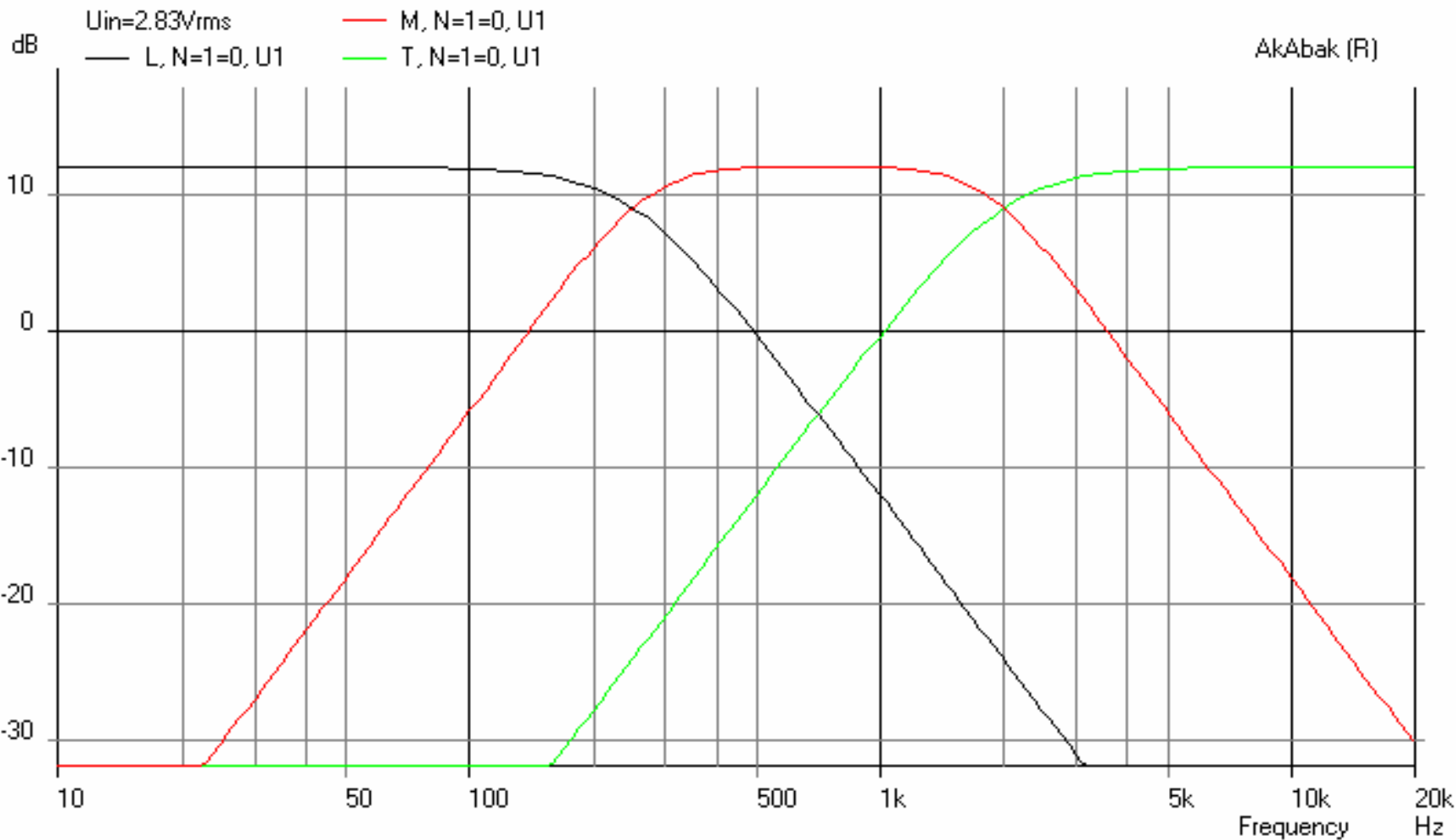

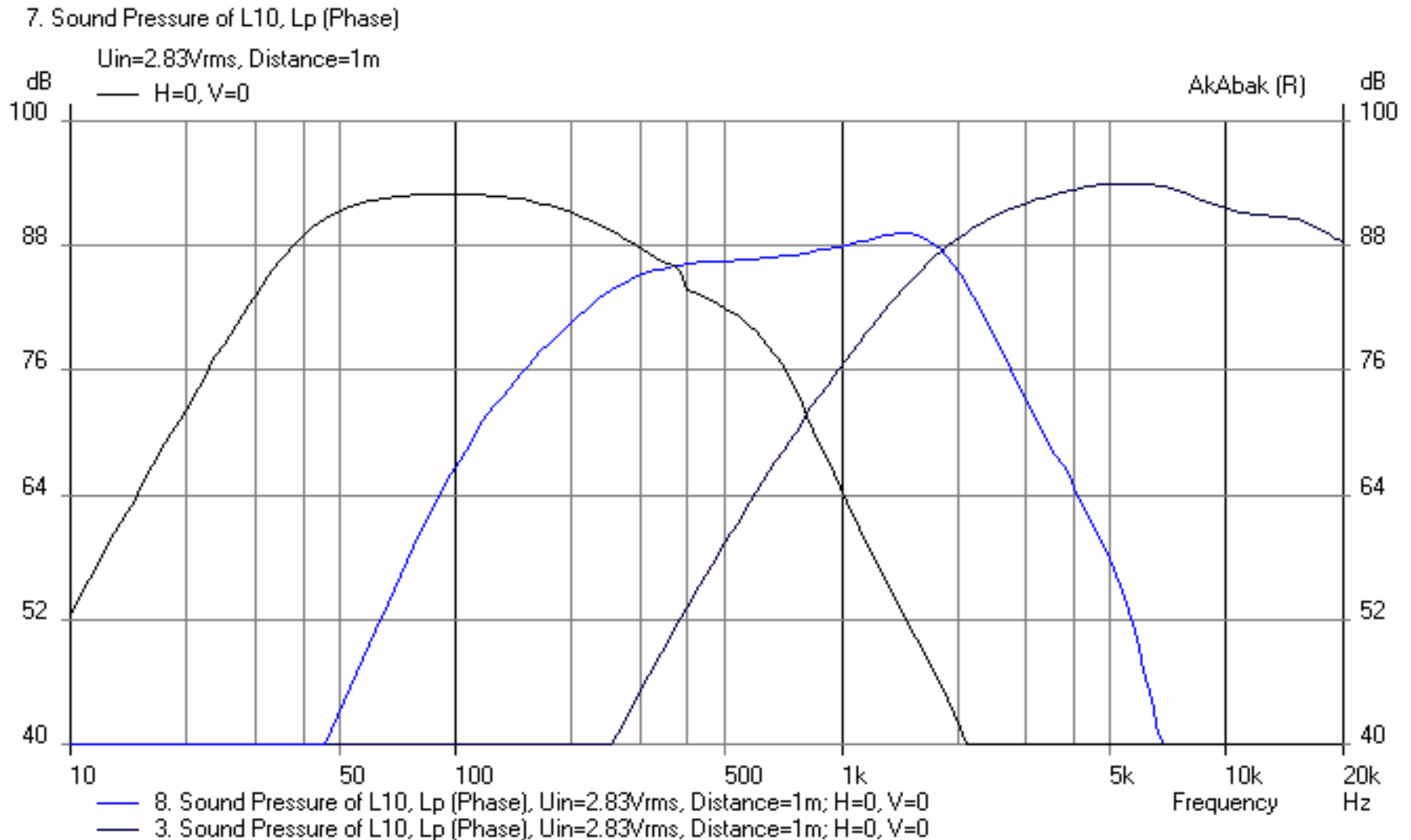
# Hladiny akustických tlakov nízkotónovej, stredotónovej a vysokotónovej po filtrácii: porovnanie




# Celková hladina akustického tlaku s použitím elektrických filtrov (súčet akustických tlakov nízkotónovej, stredotónovej a vysokotónovej)

9. Sound Pressure of L10, Lp (Phase)

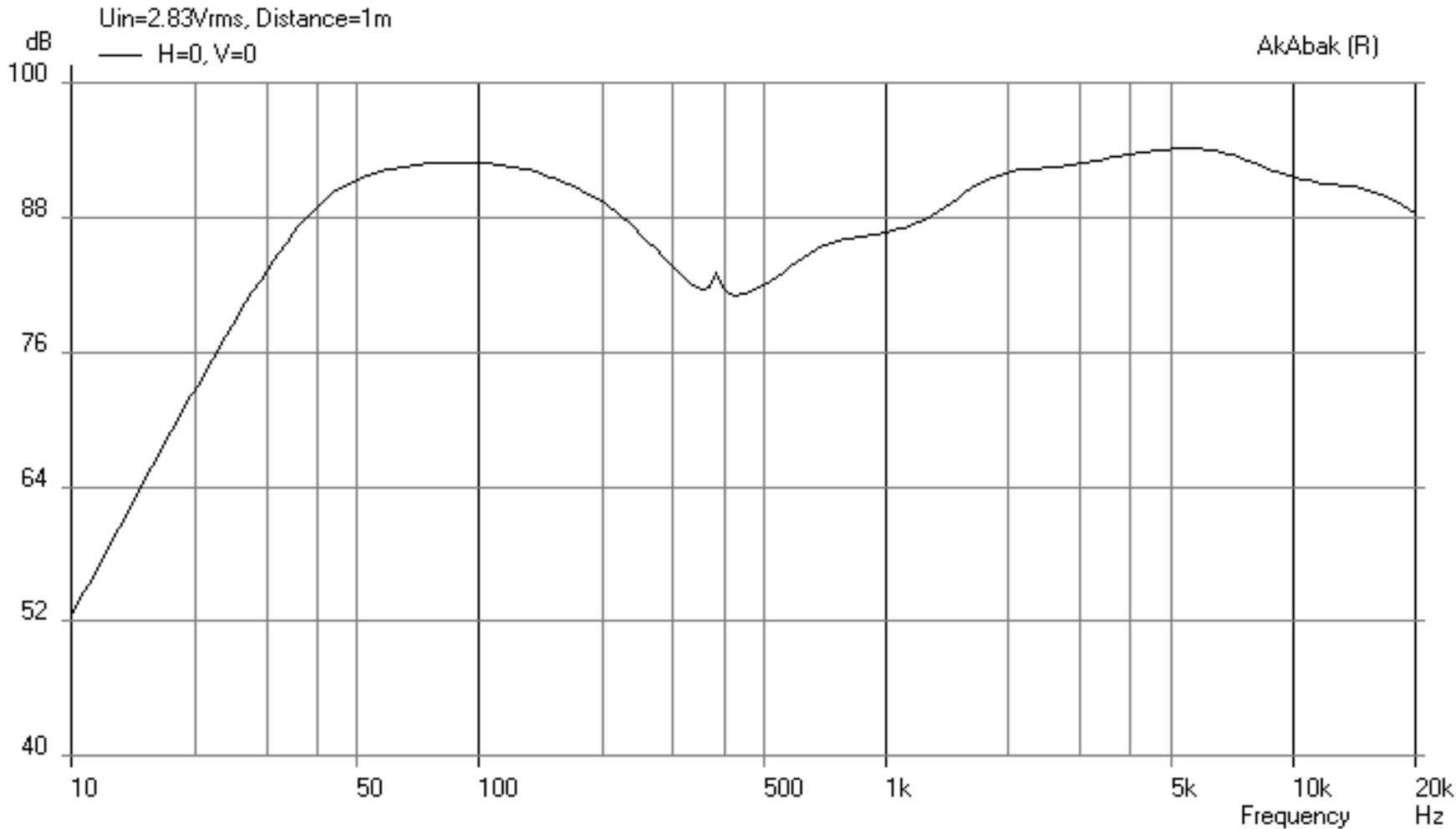

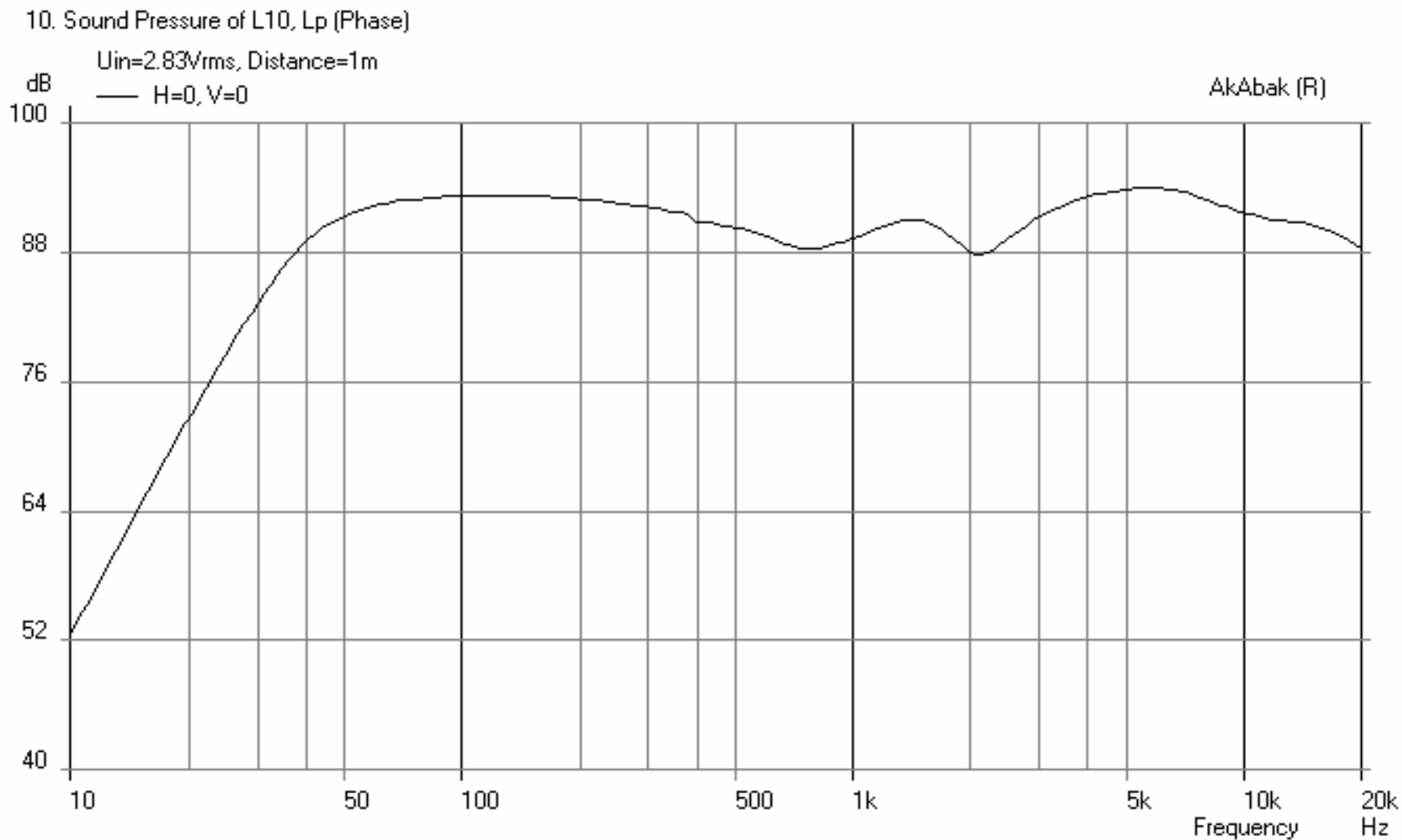
# Celková hladina akustického tlaku s použitím elektrických filtrov (súčet akustických tlakov nízkotónovej, stredotónovej a vysokotónovej, opačná polarita stredotónového reproduktora)




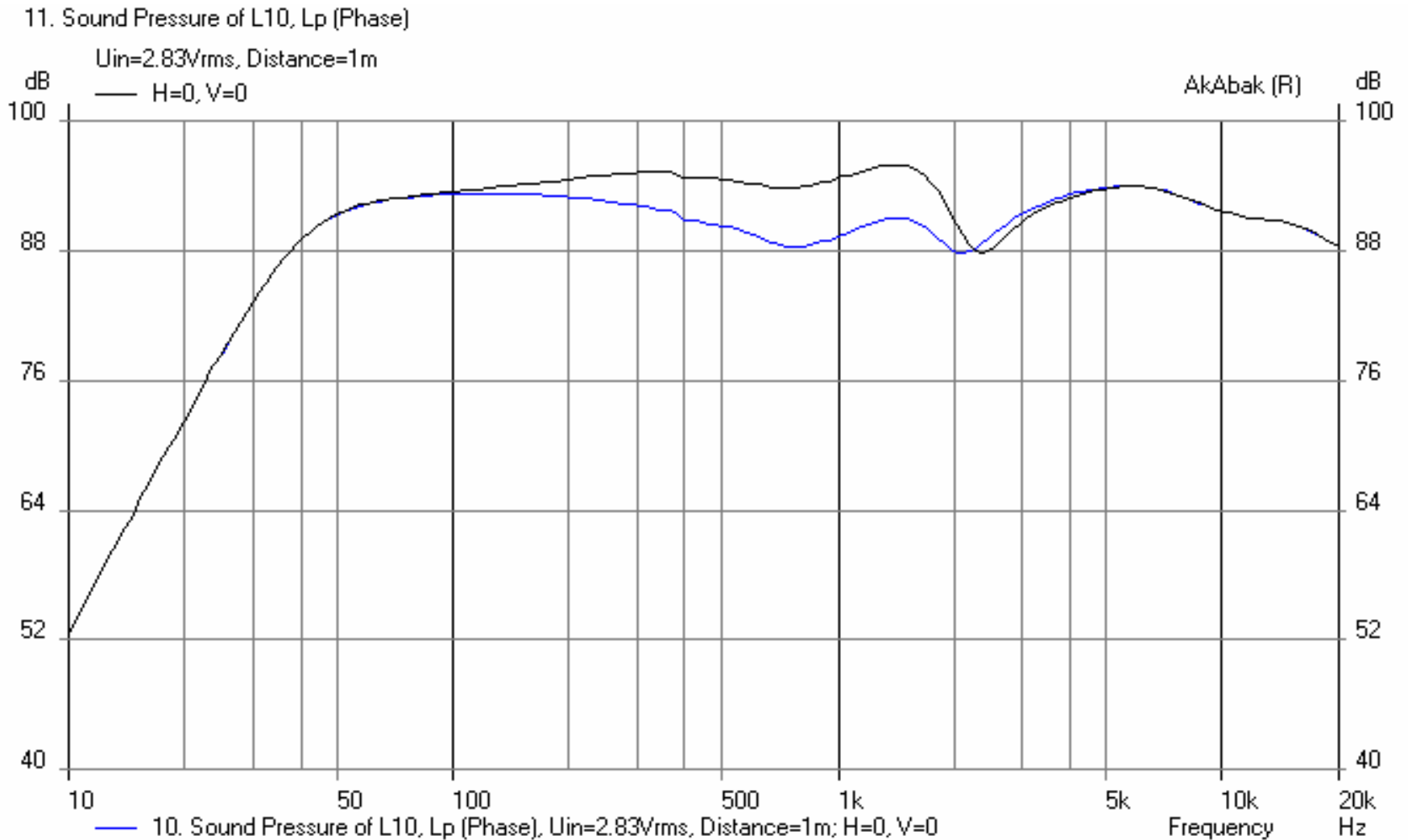
# Pridaný ďalší stredotónový reproduktor – zvýšenie citlivosti na stredných frekvenciách



## Skript

(zmena triedy filtrov na Linwitz-Riley, malá úprava medzných frekvencií)

Def\_Driver 'Woofer'

SD=350cm<sup>2</sup> dD1=5.5cm tD1=6.5cm |Cone  
fs=25Hz Vas=164L Qms=3.99  
Qes=0.3 Re=6.1ohm Le=3.08mH ExpoLe=0.618

Def\_Driver 'Midrange'

SD=55cm<sup>2</sup> dD1=3.6cm tD1=1.75cm |Cone  
fs=68Hz Vas=5L Qms=2.42  
Qes=0.74 Re=6.2ohm Le=0.31mH ExpoLe=0.618

Def\_Speaker 'Tweeter'

Meas\_Dipole  
SD=7.5cm<sup>2</sup> tD1=5.5mm t1=3.5mm |Convex Dome  
fs=550Hz Vas=17.8cm<sup>3</sup> Qms=2.425  
Bl=3.5Tm Re=4.8ohm Le=50uH ExpoLe=0.618

System 'L'

Filter 'LPF-LR2'

fo=200Hz vo=1  
{b0=1; a2=1; a1=2; a0=1; }  
Driver 'D1' Def='Woofer' Node=1=0=2=3  
Radiator 'Rad1' Def='D1' Node=2  
x=0 y=0 z=0 HAngle=0 VAngle=0  
Enclosure 'E1' Node=3  
Vb=45L Sb=350cm<sup>2</sup>  
fb=34Hz dD=10cm QD/fo=0.34 Visc=0  
x=0 y=0 z=0 HAngle=0 VAngle=0

System 'M1'

Filter 'BPF-LR2'

fo=707.106Hz vo=1  
{b2=1; a4=0.123457; a3=0.702728; a2=1.246914;  
a1=0.702728; a0=0.123457; }  
Driver 'D2' Def='Midrange' Node=0=1=4=5  
Radiator 'Rad1' Def='D2' Node=4  
x=0 y=0 z=0 HAngle=0 VAngle=0  
Enclosure 'E2' Node=5  
Vb=3.2L Sb=55cm<sup>2</sup>

System 'M2'

Filter 'BPF-LR2'

fo=707.106Hz vo=1  
{b2=1; a4=0.123457; a3=0.702728; a2=1.246914;  
a1=0.702728; a0=0.123457; }  
Driver 'D2' Def='Midrange' Node=0=1=4=5  
Radiator 'Rad1' Def='D2' Node=4  
x=0 y=10cm z=0 HAngle=0 VAngle=0  
Enclosure 'E2' Node=5  
Vb=3.2L Sb=55cm<sup>2</sup>


System 'T'

Filter 'HPF-LR2'

fo=1.5kHz vo=1  
{b2=1; a2=1; a1=2; a0=1; }  
Speaker 'Sp1' Def='Tweeter' Node=0=1  
x=0 y=0 z=0 HAngle=0 VAngle=0

# AFCH flitrov Linkwitz-Riley 2. rádu

26. Voltage of L10, Level (Phase)

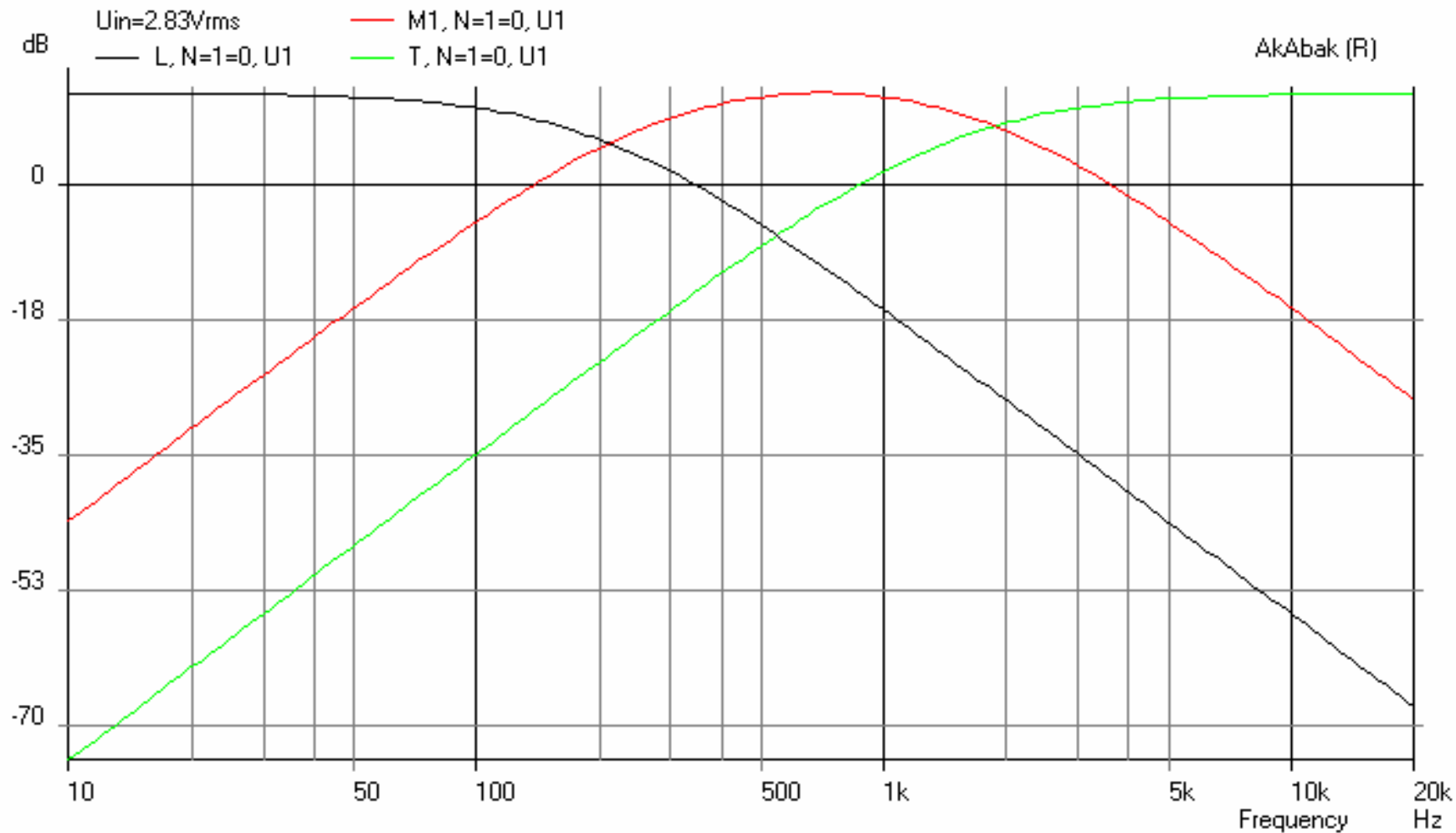


# Hladina akustického tlaku sústavy s použitím filtrov triedy Linkwitz-Riley

27. Sound Pressure of L10, Lp (Phase)

U<sub>in</sub>=2.83V<sub>rms</sub>, Distance=1m

— H=0, V=0

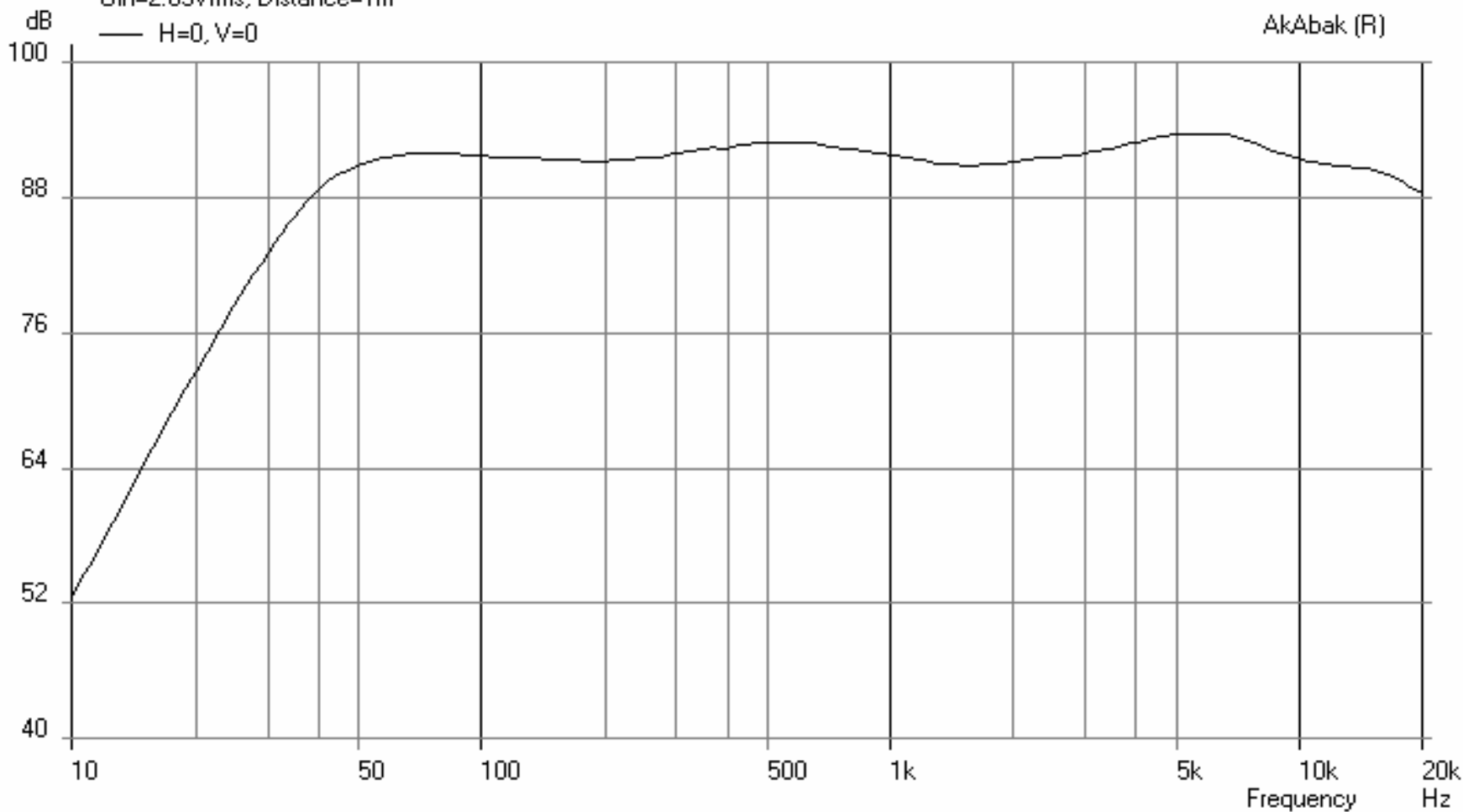

# Syntéza pasívnych filtrov

- ...

# Syntéza DPF: Filter/LCR-Synthesis

## Synthesis of Polynomial Filters with Passive Elements

Transfer function

+1

$1*s^2 + 2*s + 1$

**RL** - loading  
resistor ..ohm..

6.1ohm

**QL** - coils  
quality factor

**fo** - filter  
frequency ..Hz..

200Hz

**yo** -  
amplification

1

First node  
number

1

Network  
type 1

Get from  
script

Network  
type 2

Copy and  
close

Copy including RL

**Network**

Max. L: 9.708mH

Max. C: 65.227uF

Damp.:

Coil Node=1=2 L=9.708mH  
Capacitor Node=2=0 C=65.227uF  
Resistor 'RL' Node=2=0 R=6.1ohm

## System 'L'

Coil Node=1=2 L=9.708mH

Capacitor Node=2=0 C=65.227uF

### SynthesisInfo

Passive FirstNode=1 RL=6.1ohm QL=0

fo=200Hz vo=1

{b0=1;

a2=1; a1=2; a0=1; }

Driver 'D1' Def='Woofers' Node=2=0=3=4

Radiator 'Rad1' Def='D1' Node=3

x=0 y=0 z=0 HAngle=0 VAngle=0


Enclosure 'E1' Node=4

Vb=45L Sb=350cm<sup>2</sup>


fb=34Hz dD=10cm QD/fo=0.34 Visc=0

x=0 y=0 z=0 HAngle=0 VAngle=0

# Nízkotónová část'

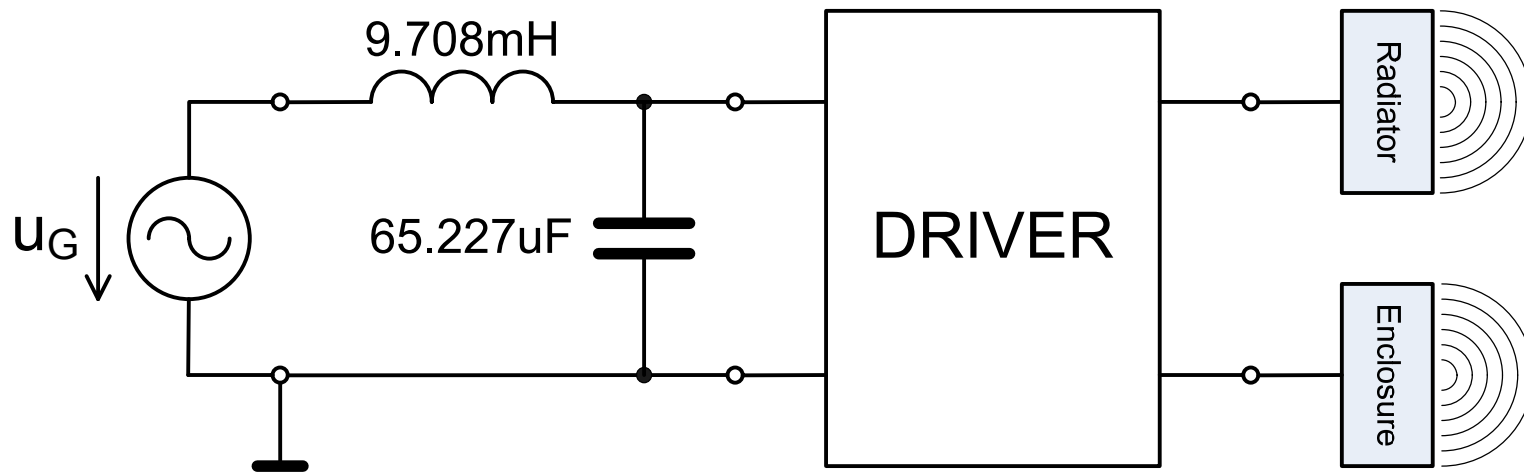

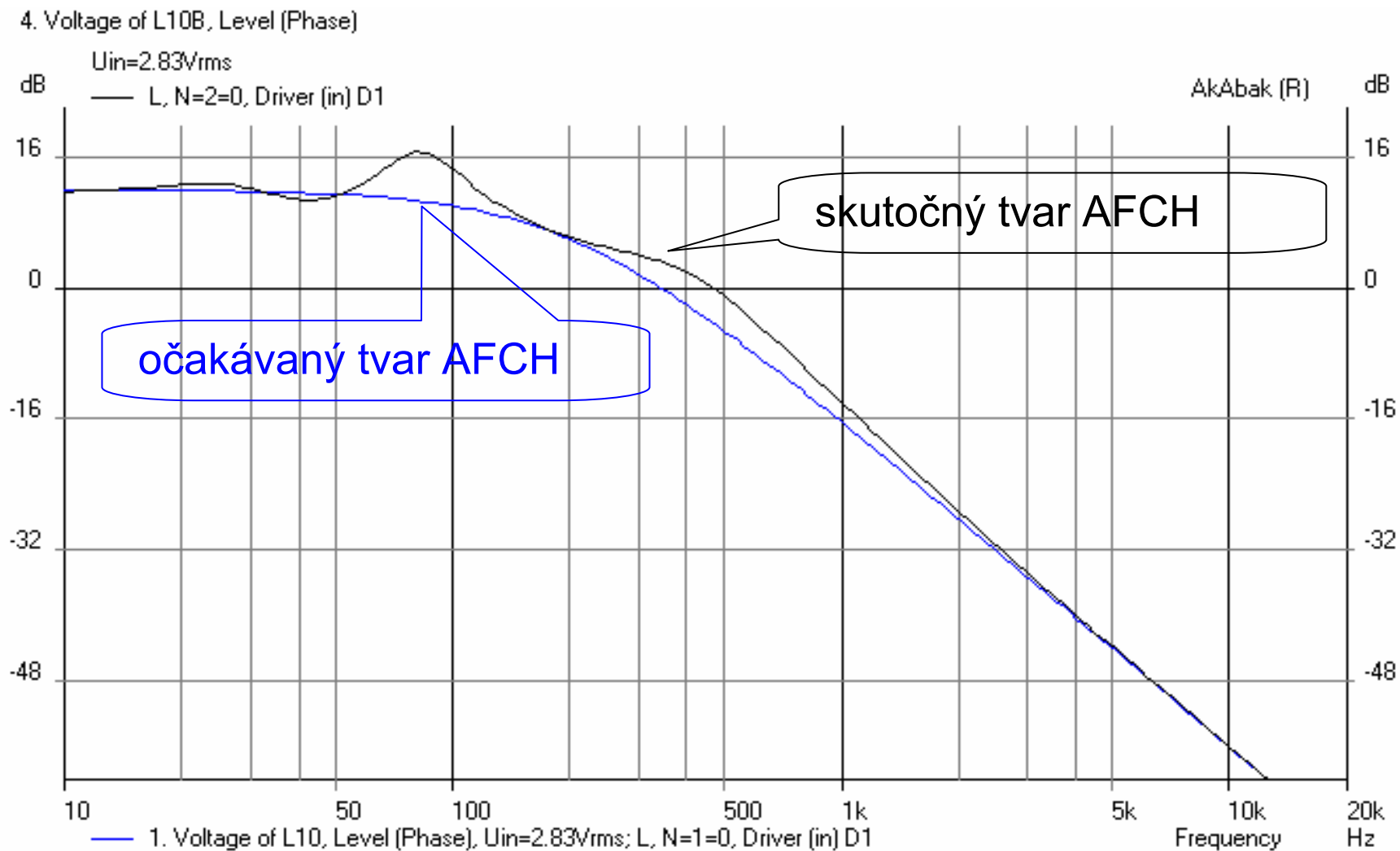
# Napätie na výstupe DP filtra: ukážka vplyvu skutočnej impedancie reproduktora na AFCH filtra





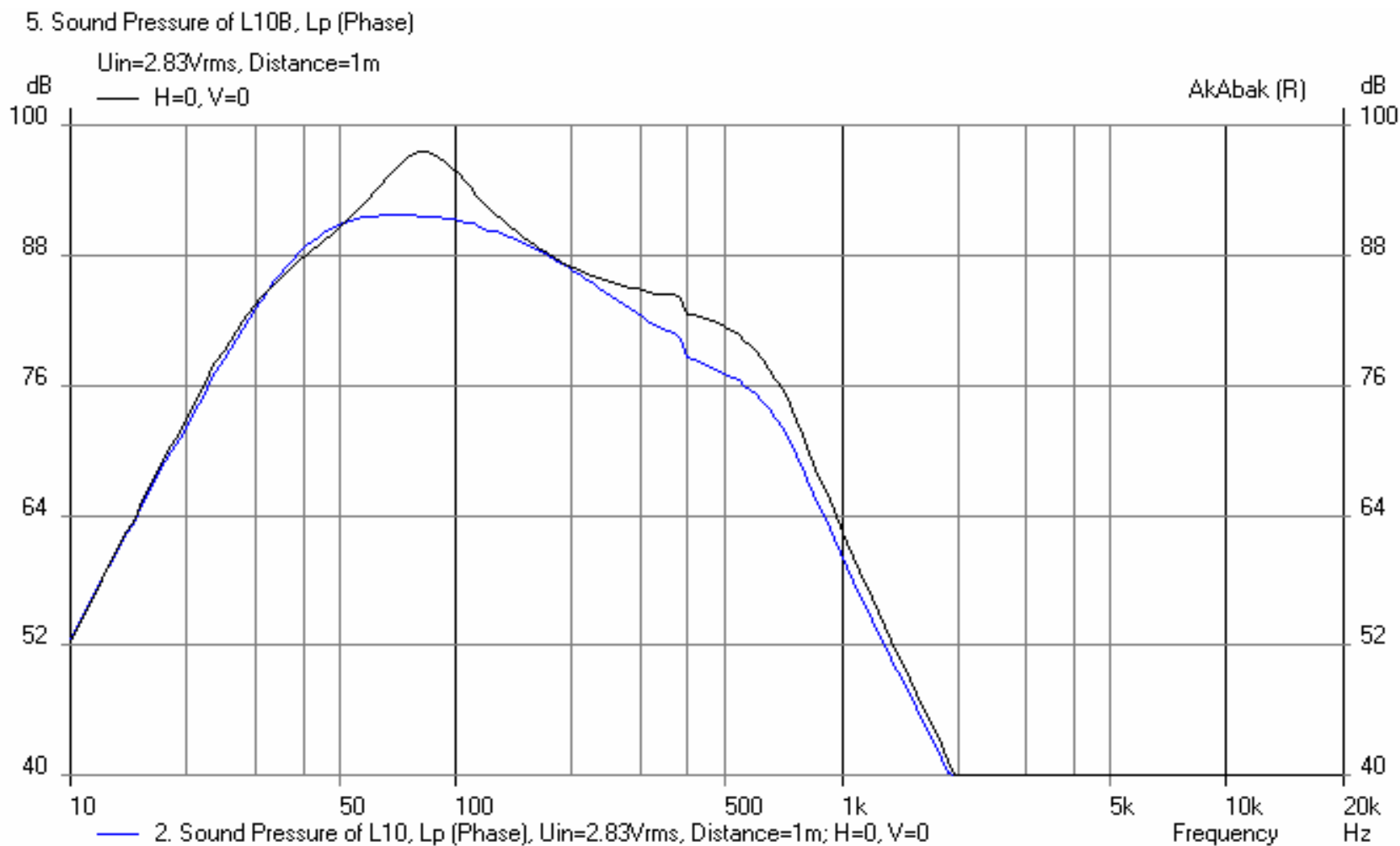
# Hladina akustického tlaku nízkotónovej časti po filtrácii skutočným filtrom (záťažou je impedancia reproduktora)



# Stredotónová časť

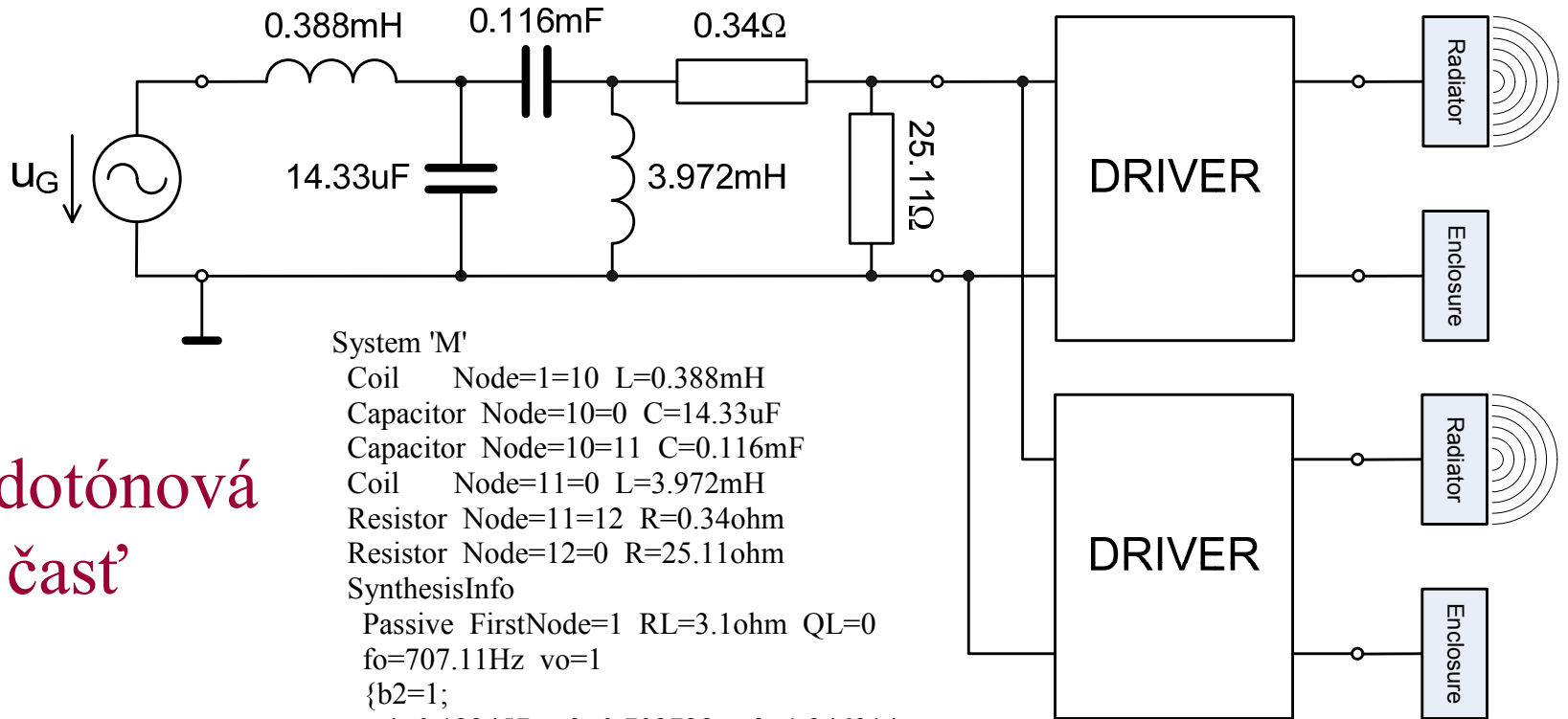


System 'M'  
 Coil Node=1=10 L=0.388mH  
 Capacitor Node=10=0 C=14.33uF  
 Capacitor Node=10=11 C=0.116mF  
 Coil Node=11=0 L=3.972mH  
 Resistor Node=11=12 R=0.34ohm  
 Resistor Node=12=0 R=25.11ohm  
 SynthesisInfo  
 Passive FirstNode=1 RL=3.1ohm QL=0  
 fo=707.11Hz vo=1  
 {b2=1;  
 a4=0.123457; a3=0.702728; a2=1.246914;  
 a1=0.702728; a0=0.123457; }

Driver 'D2' Def='Midrange' Node=0=12=15=16  
 Radiator 'Rad1' Def='D2' Node=15  
 x=0 y=0 z=0 HAngle=0 VAngle=0  
 Enclosure 'E2' Node=16  
 Vb=3.2L Sb=55cm<sup>2</sup>

Driver 'D2' Def='Midrange' Node=0=12=17=18  
 Radiator 'Rad1' Def='D2' Node=17  
 x=0 y=10cm z=0 HAngle=0 VAngle=0  
 Enclosure 'E2' Node=18  
 Vb=3.2L Sb=55cm<sup>2</sup>


# Napätie na výstupe P filtra: ukážka vplyvu skutočnej impedancie reproduktora na AFCH filtra

6. Voltage of L10B, Level (Phase)

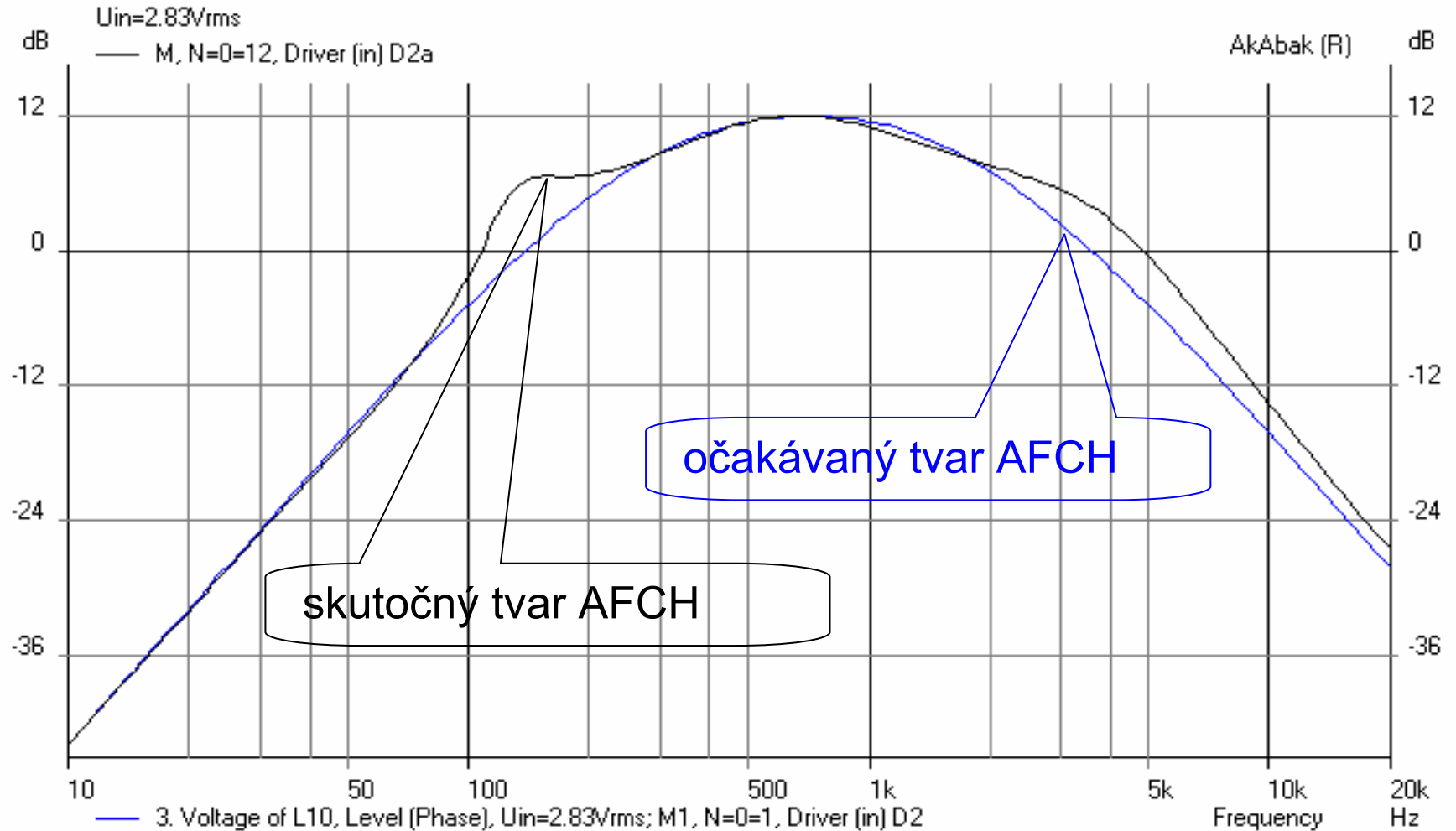

# Hladina akustického tlaku stredotónovej časti po filtrácii skutočným filtrom (záťažou je impedancia reproduktora)

## 7. Sound Pressure of L10B, Lp (Phase)

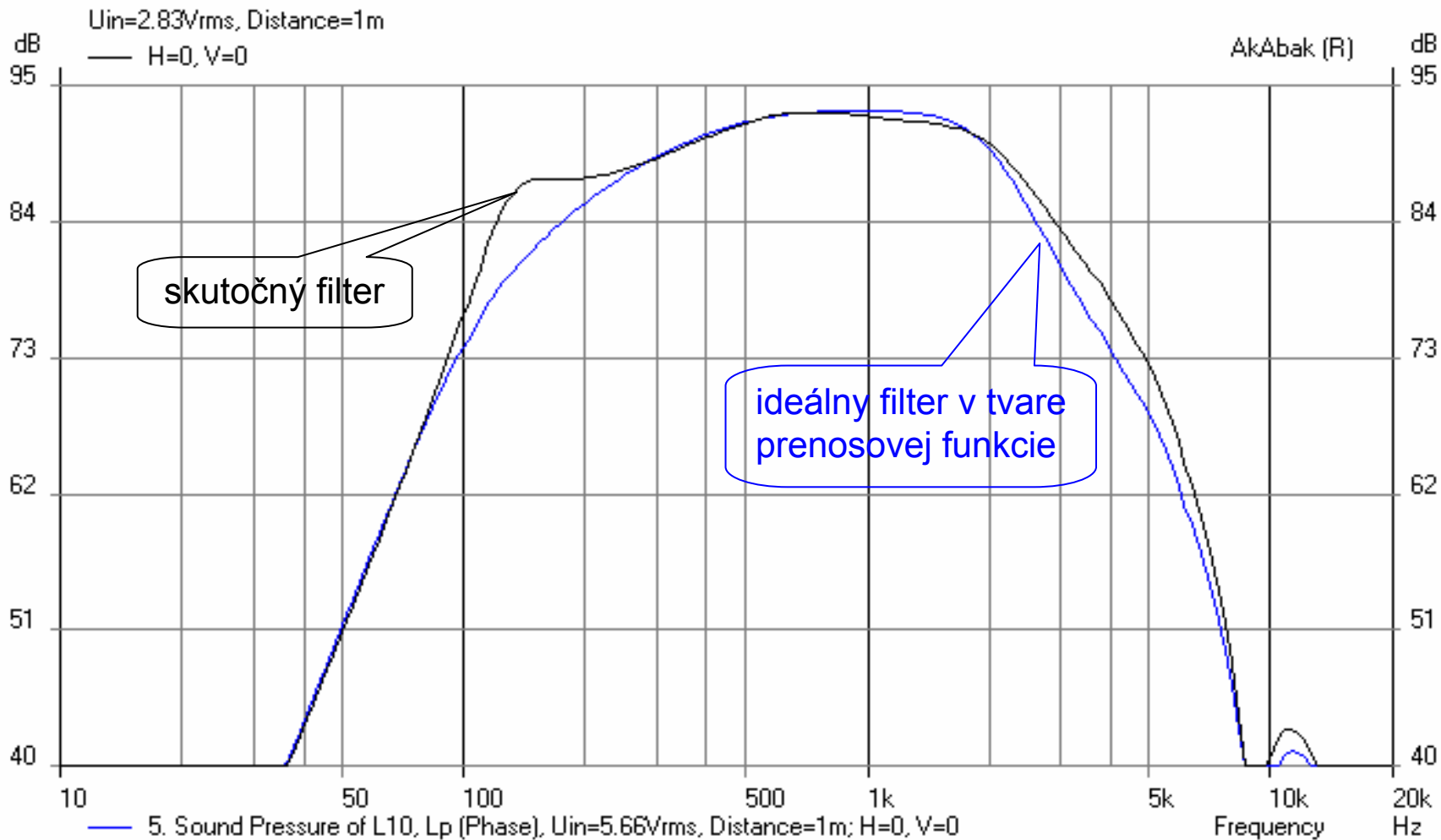

System 'T'

Capacitor Node=1=20 C=11.052uF

Coil Node=20=0 L=1.019mH

SynthesisInfo

Passive FirstNode=1 RL=4.8ohm QL=0

fo=1.5kHz vo=1


{b2=1;

a2=1; a1=2; a0=1; }


Speaker 'Sp1' Def='Tweeter' Node=0=20

x=0 y=0 z=0 HAngle=0 VAngle=0


# Vysokotónová časť

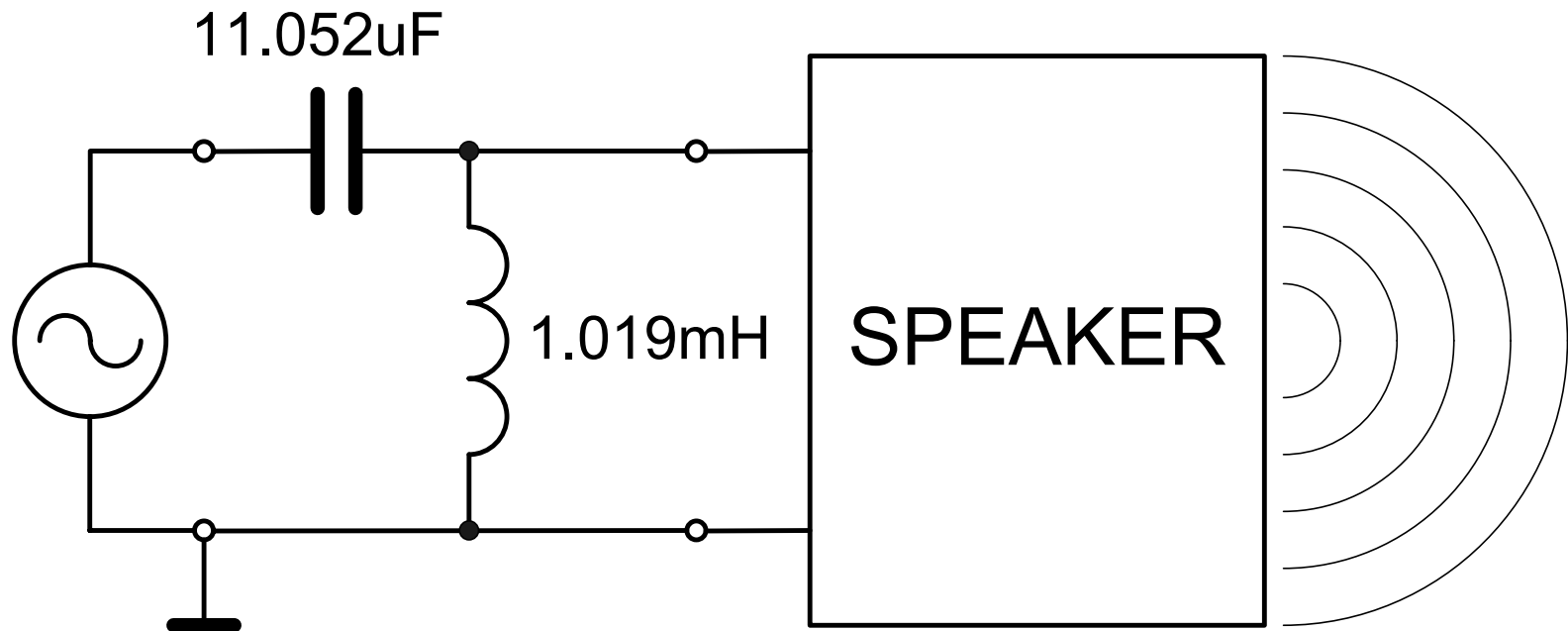
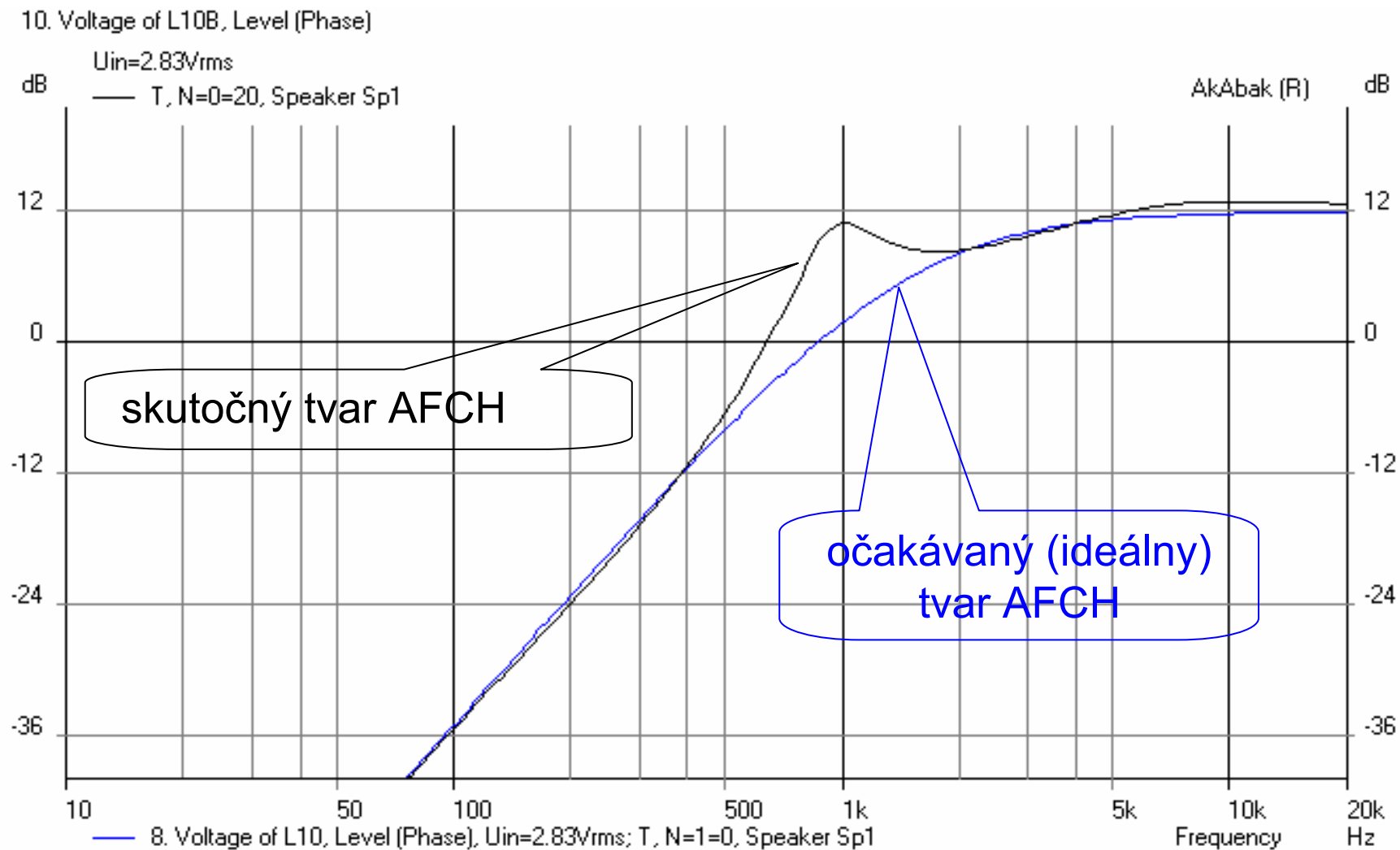
# Napätie na výstupe HP filtra: ukážka vplyvu skutočnej impedancie reproduktora na AFCH filtra


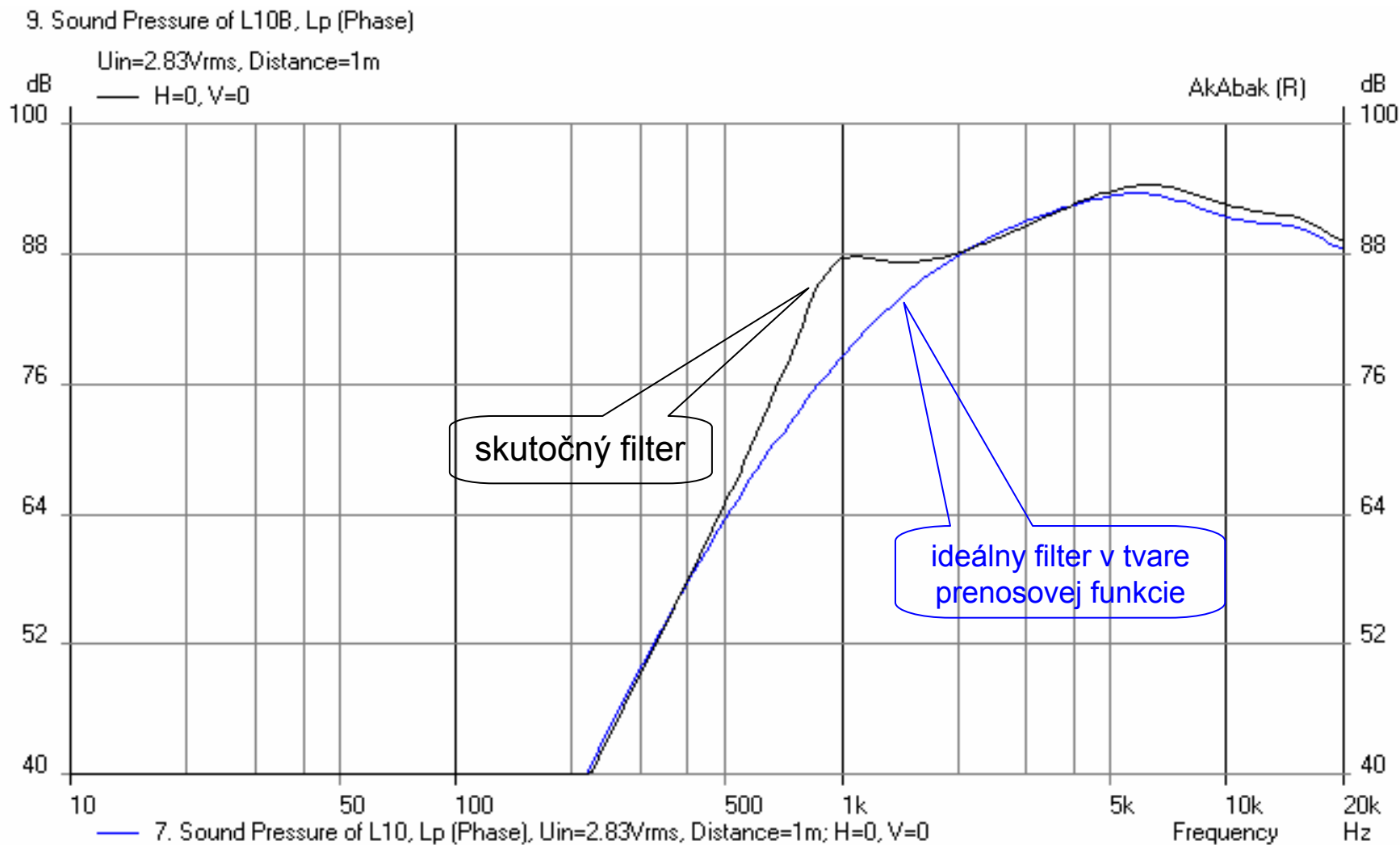
# Hladina akustického tlaku vysokotónovej časti po filtrácii skutočným filtrom (zát'azou je impedancia reproduktora)



### Def\_Driver 'Woofers'

SD=350cm<sup>2</sup> dD1=5.5cm tD1=6.5cm |Cone  
fs=25Hz Vas=164L Qms=3.99  
Qes=0.3 Re=6.1ohm Le=3.08mH ExpoLe=0.618

### Def\_Driver 'Midrange'

SD=55cm<sup>2</sup> dD1=3.6cm tD1=1.75cm |Cone  
fs=68Hz Vas=5L Qms=2.42  
Qes=0.74 Re=6.2ohm Le=0.31mH ExpoLe=0.618

### Def\_Speaker 'Tweeter'

Meas\_Dipole  
SD=7.5cm<sup>2</sup> tD1=5.5mm t1=3.5mm |Convex Dome  
fs=550Hz Vas=17.8cm<sup>3</sup> Qms=2.425  
Bl=3.5Tm Re=4.8ohm Le=50uH ExpoLe=0.618

### System 'L'

Coil Node=1=2 L=9.708mH  
Capacitor Node=2=0 C=65.227uF  
SynthesisInfo  
Passive FirstNode=1 RL=6.1ohm QL=0  
fo=200Hz vo=1  
{b0=1;  
a2=1; a1=2; a0=1; }  
Driver 'D1' Def='Woofers' Node=2=0=3=4  
Radiator 'Rad1' Def='D1' Node=3  
x=0 y=0 z=0 HAngle=0 VAngle=0  
Enclosure 'E1' Node=4  
Vb=45L Sb=350cm<sup>2</sup>  
fb=34Hz dD=10cm QD/fo=0.34 Visc=0  
x=0 y=0 z=0 HAngle=0 VAngle=0

• • •

### System 'M'




Coil Node=1=10 L=0.388mH  
Capacitor Node=10=0 C=14.33uF  
Capacitor Node=10=11 C=0.116mF  
Coil Node=11=0 L=3.972mH  
Resistor Node=11=12 R=0.34ohm  
Resistor Node=12=0 R=25.11ohm  
SynthesisInfo  
Passive FirstNode=1 RL=3.1ohm QL=0  
fo=707.11Hz vo=1  
{b2=1;  
a4=0.123457; a3=0.702728; a2=1.246914;  
a1=0.702728; a0=0.123457; }  
Driver 'D2a' Def='Midrange' Node=0=12=15=16  
Radiator 'Rad1' Def='D2a' Node=15  
x=0 y=0 z=0 HAngle=0 VAngle=0  
Enclosure 'E2' Node=16  
Vb=3.2L Sb=55cm<sup>2</sup>  
Driver 'D2b' Def='Midrange' Node=0=12=17=18  
Radiator 'Rad1' Def='D2b' Node=17  
x=0 y=10cm z=0 HAngle=0 VAngle=0  
Enclosure 'E2' Node=18  
Vb=3.2L Sb=55cm<sup>2</sup>

### System 'T'

Capacitor Node=1=20 C=11.052uF  
Coil Node=20=0 L=1.019mH  
SynthesisInfo  
Passive FirstNode=1 RL=4.8ohm QL=0  
fo=1.5kHz vo=1  
{b2=1;  
a2=1; a1=2; a0=1; }  
Speaker 'Sp1' Def='Tweeter' Node=20=0  
x=0 y=0 z=0 HAngle=0 VAngle=0




# Celá sústava

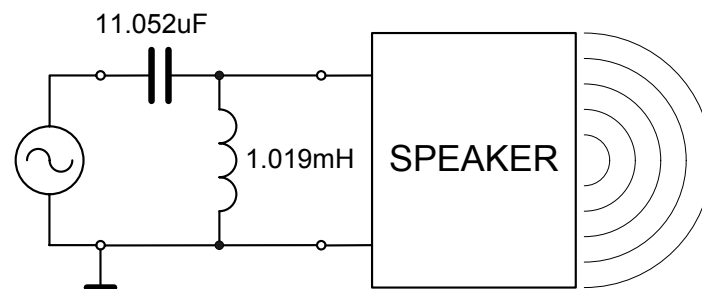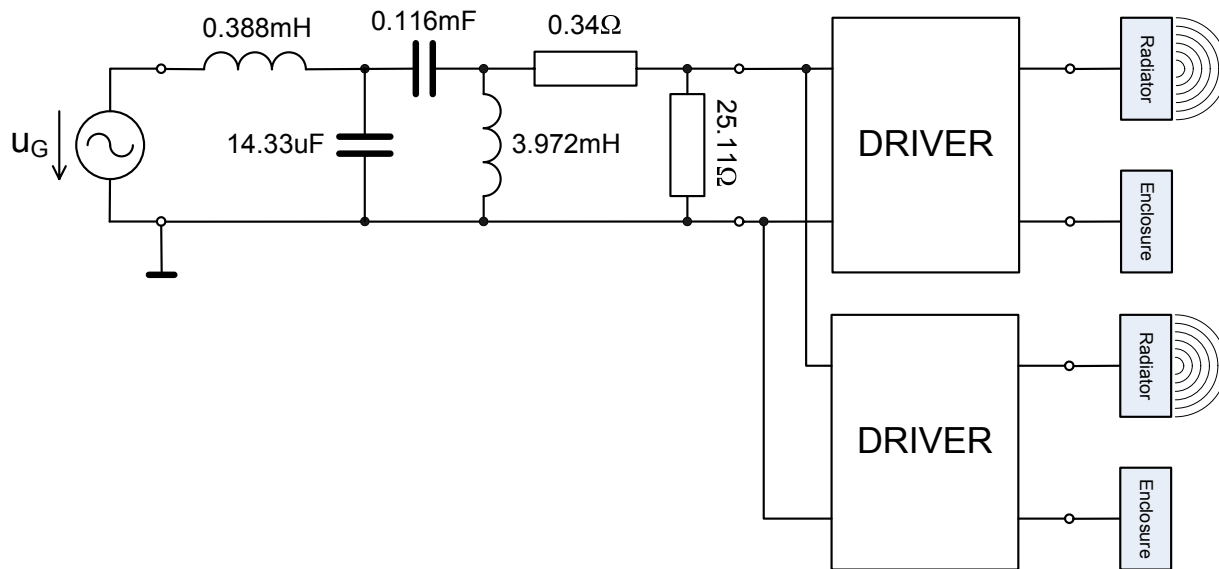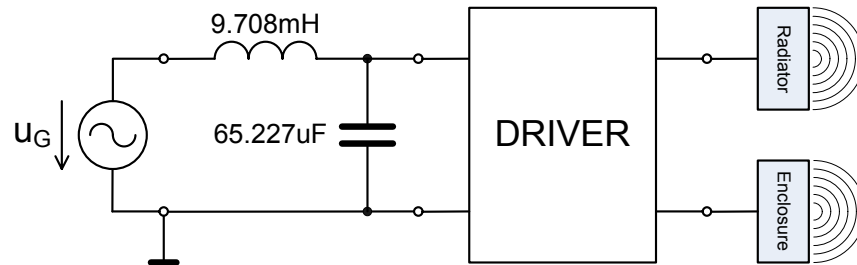


# Napätia na výstupe elektrických filtrov

11. Voltage of L10B, Level (Phase)

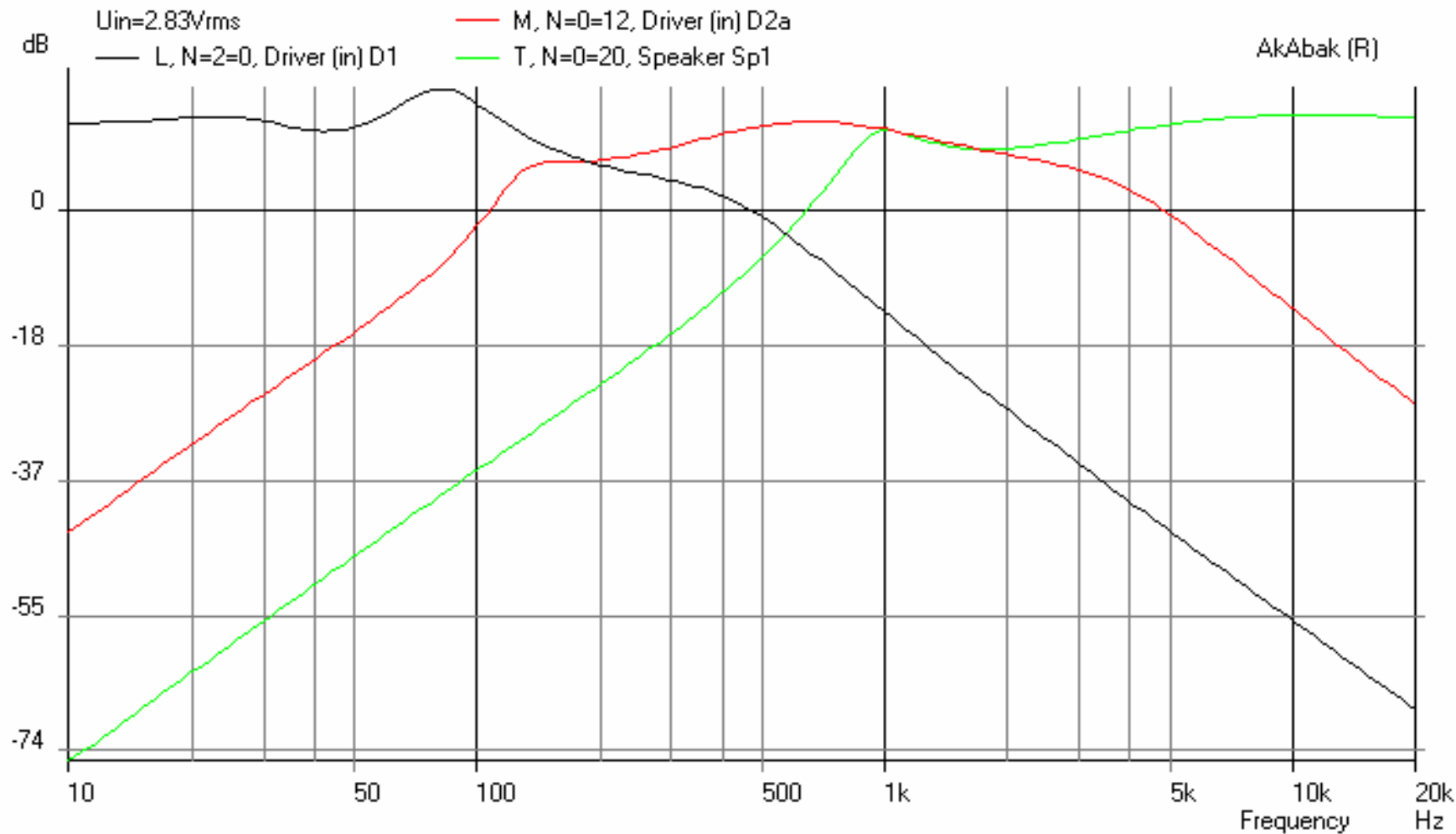


# Hladina akustického tlaku sústavy

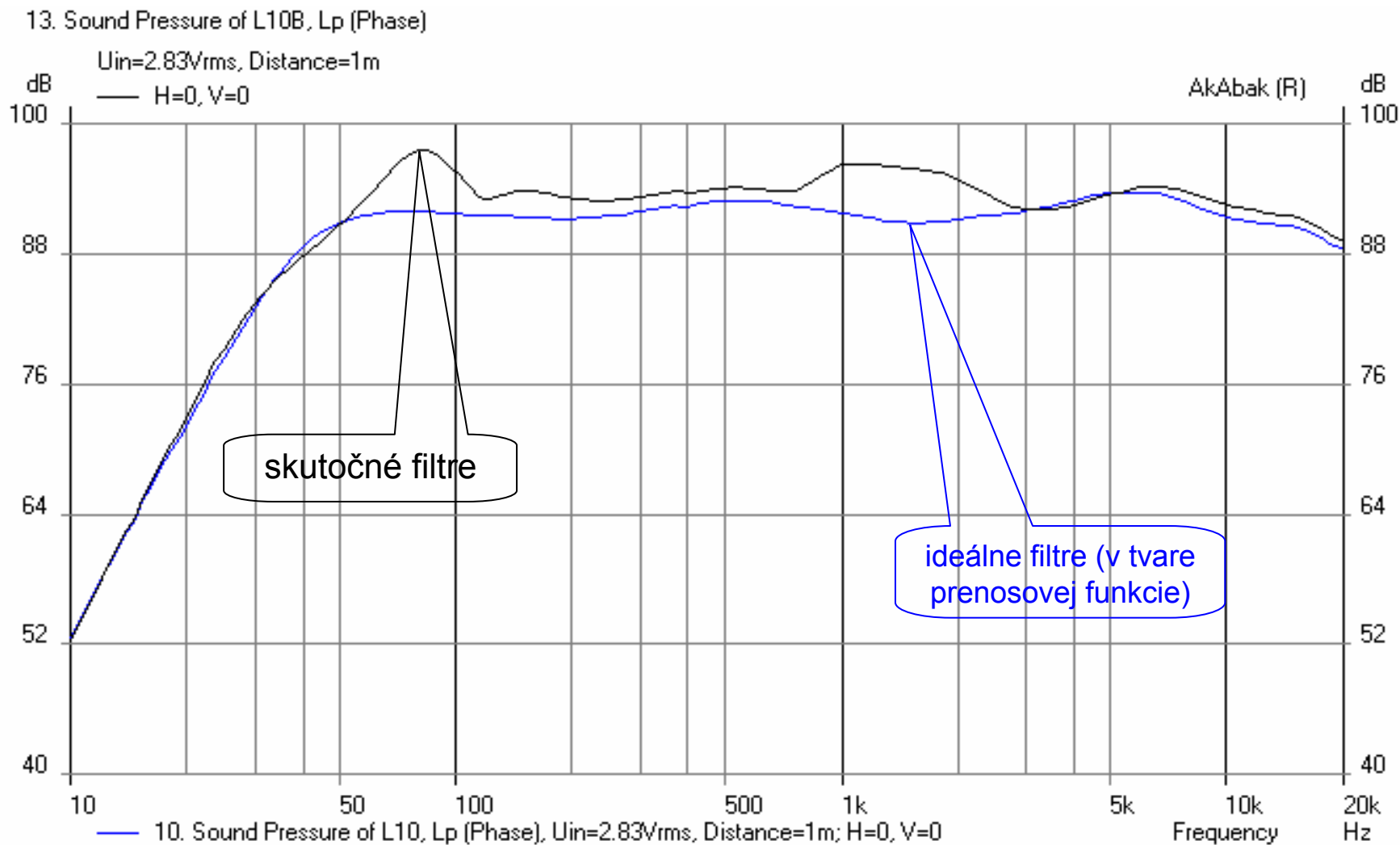
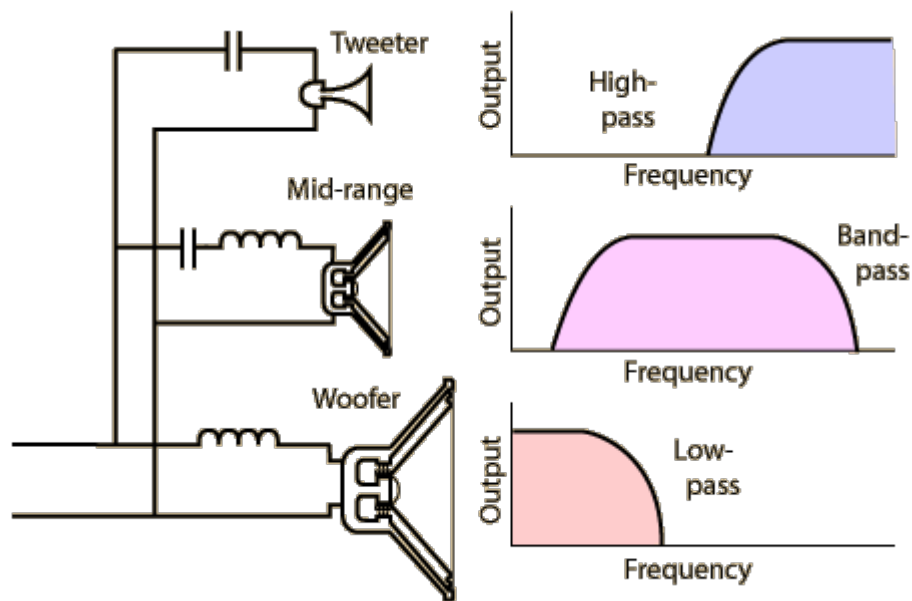
# Úloha výhybky

- Elektronické výhybky sú elektrické filtre, ktoré delia vstupný audiosignál do frekvenčných pásiem, vhodných na reprodukciu jednotlivými reproduktormi sústavy:
  - Dvojpásmová sústava – dolnopriepustný filter (DP) a hornopriepustný filter (HP)
  - Trojpásmová sústava – DP, pásmový filter (PP), HP
- Elektrické zapojenie
  - Sériové – filter a reproduktor v rámci pásma
  - Paralelné – pásma voči sebe



# Deliaca frekvencia


- Je to frekvencia, ktorá vymedzuje hranicu medzi frekvenčnými pásmami dvoch "susedných" reproduktorov
- Pri deliacej frekvencii by mali obidva reproduktory emitovať rovnaký "osový" akustický tlak
- Typické hodnoty:
  - Dvojpásmová sústava v rozmedzí 1.5-2 kHz
  - Trojpásmová sústava v rozmedzí 300-800 Hz resp. 3-5 khz
- Presnejší odhad deliacej frekvencie:
  - Mala by byť zvolená tak, aby reproduktor neemitoval akustické vlnenie pri frekvencii väčšej, ako je frekvencia, pri ktorej  $kR=1$  ( $k$  – vlnové číslo,  $R$  – polomer plochy ústia membrány)
  - Ak chceme reproduktor používať pri frekvencii vyššej, je potrebné osobitnú pozornosť venovať výberu (resp. návrhu) vhodného reproduktora (najmä materiál membrány)

# Medzná frekvencia

- Medzná frekvencia výhybkového filtra je bežne špecifikovaná ako frekvencia, pri ktorej AFCH filtra klesá o 3 dB, v špeciálnych prípadoch o 6dB:
  - DP má hornú medznú frekvenciu
  - HP má dolnú medznú frekvenciu
  - PP má dolnú aj hornú medznú frekvenciu
- Skutočná medzná frekvencia pásma sa môže odlišovať od teoreticky vypočítanej:
  - Rozdiel medzi menovitým odporom a skutočnou impedanciou reproduktora
  - Interakcia prenosových funkcií filtra a reproduktora
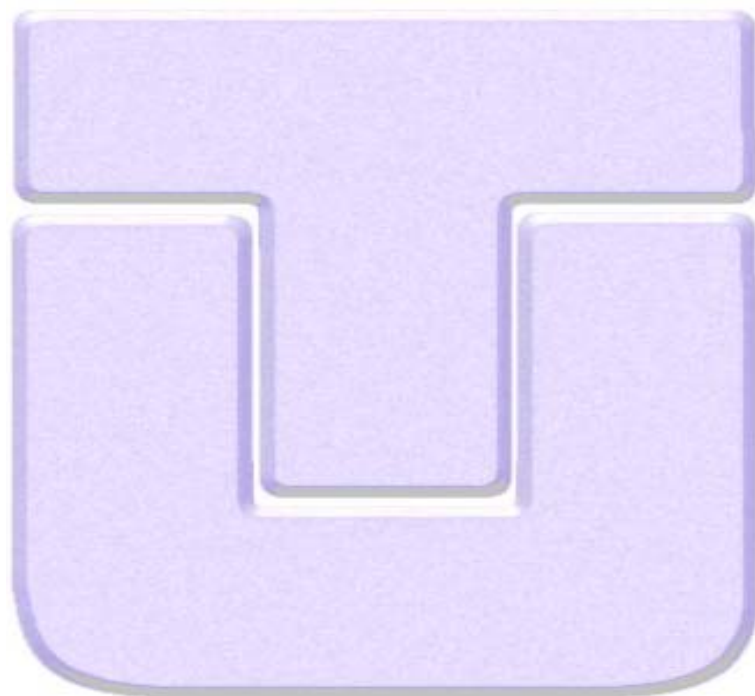
# Rád, typ a trieda filtra

- Rád filtra – sklon AFCH v pásme zádrže
  - 1. rád – 6dB/okt. resp. 10dB/dek.
  - 2. rád – 12dB/okt. resp. 20dB/dek.
  - 3. rád - 18dB/okt. resp. 30dB/dek.
  - N-tý rád -  $n \times 6$ dB/okt. resp.  $n \times 10$ dB/dek.
- Typ filtra:
  - Dolný priepust
  - Horný priepust
  - Pásmový priepust
  - Pásmová zádrž
- Trieda filtra
  - Butterworth
  - Čebyšev
  - Bessel
  - Linkwitz-Riley
  - ...





# Pasívne filtre 1. rádu


$$T_w(s) = \frac{1}{1 + s/\omega_w}$$

$$\begin{aligned}
 T_m(s) &= \frac{s/\omega_{m1}}{1 + s/\omega_{m1}} \frac{1}{1 + s/\omega_{m2}} = \frac{s/\omega_{m1}}{1 + s\left(\frac{1}{\omega_{m1}} + \frac{1}{\omega_{m2}}\right) + s^2 \frac{1}{\omega_{m1}\omega_{m2}}} = \frac{s/\omega_{m1}}{1 + s\left(\frac{\omega_{m1} + \omega_{m2}}{\omega_{m1}\omega_{m2}}\right) + s^2 \frac{1}{\omega_{m1}\omega_{m2}}} \\
 &= \frac{s/\omega_{m1}}{1 + s\left(\frac{\omega_{m1} + \omega_{m2}}{\omega_{m1}\omega_{m2}}\right) + s^2 \frac{1}{\omega_{m1}\omega_{m2}}} = \frac{\sqrt{\omega_{m1}\omega_{m2}} \sqrt{\omega_{m2}}}{\omega_{m1} + \omega_{m2} \sqrt{\omega_{m1}}} \frac{s \frac{1}{\sqrt{\omega_{m1}\omega_{m2}}}}{\frac{\omega_{m1} + \omega_{m2}}{\sqrt{\omega_{m1}\omega_{m2}}} + s \frac{1}{\sqrt{\omega_{m1}\omega_{m2}}} + s^2 \frac{1}{\omega_{m1}\omega_{m2}} \frac{\omega_{m1} + \omega_{m2}}{\sqrt{\omega_{m1}\omega_{m2}}}} \\
 &= \frac{\sqrt{\omega_{m1}\omega_{m2}} \sqrt{\omega_{m2}}}{\omega_{m1} + \omega_{m2} \sqrt{\omega_{m1}}} \frac{s \frac{1}{\sqrt{\omega_{m1}\omega_{m2}}}}{\frac{\omega_{m1} + \omega_{m2}}{\omega_{m1} + \omega_{m2} \sqrt{\omega_{m1}}} + s \frac{1}{\sqrt{\omega_{m1}\omega_{m2}}} + s^2 \frac{1}{\omega_{m1}\omega_{m2}} \frac{\omega_{m1} + \omega_{m2}}{\omega_{m1} + \omega_{m2} \sqrt{\omega_{m1}}}}
 \end{aligned}$$

$$T_t(s) = \frac{s/\omega_t}{1 + s/\omega_t}$$

$\omega_w, \omega_{m1}, \omega_{m2}, \omega_{wt}$  – medzné frekvencie (-3dB)

# Pasívna výhybka 1. rádu

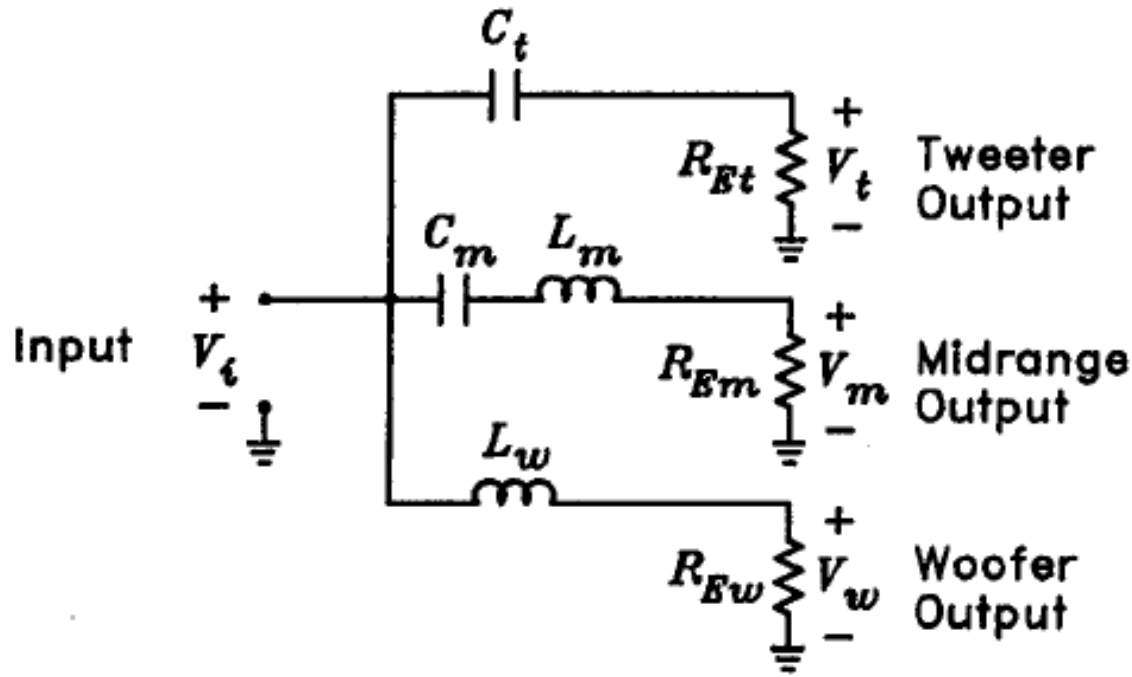

$$L_w = \frac{R_{Ew}}{2\pi f_w}$$

$$C_m = \frac{1}{2\pi f_{m1} R_{Em}}$$


$$L_m = \frac{R_{Em}}{2\pi f_{m2}}$$

$$C_t = \frac{1}{2\pi f_t R_{Et}}$$

$$T_w(s) = \frac{1}{1 + s/\omega_w} \quad T_m(s) = \frac{s/\omega_{m1}}{1 + s/\omega_{m1}} \frac{1}{1 + s/\omega_{m2}} \quad T_t(s) = \frac{s/\omega_t}{1 + s/\omega_t}$$

$\omega_w, \omega_{m1}, \omega_{m2}, \omega_{wt}$  – medzné frekvencie (-3dB)

# Pasívna výhybka 2. rádu

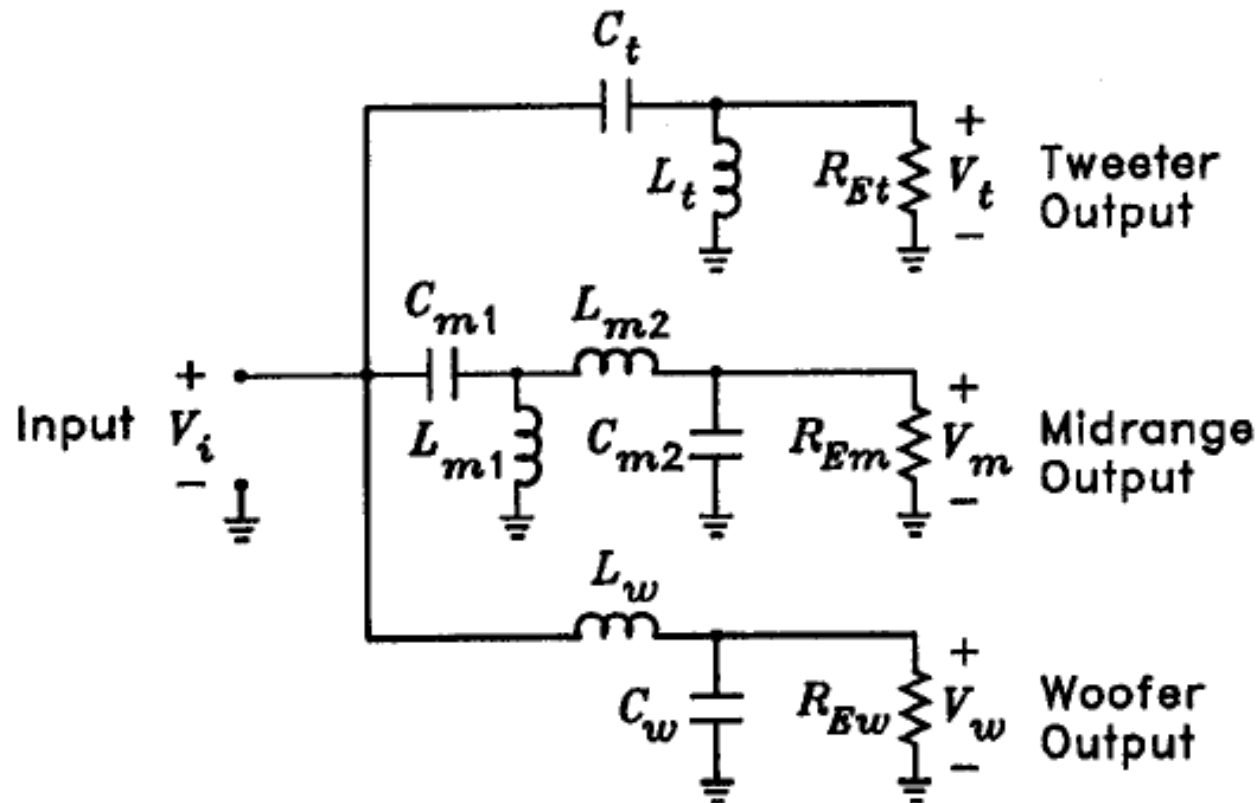

$$T_w(s) = \frac{1}{(s/\omega_w)^2 + (1/Q_w)(s/\omega_w) + 1} \quad (9.3)$$

$$T_m(s) = \frac{(s/\omega_{m1})^2}{(s/\omega_{m1})^2 + (1/Q_{m1})(s/\omega_{m1}) + 1} \times \frac{1}{(s/\omega_{m2})^2 + (1/Q_{m2})(s/\omega_{m2}) + 1} \quad (9.4)$$

$$T_t(s) = \frac{(s/\omega_t)^2}{(s/\omega_t)^2 + (1/Q_t)(s/\omega_t) + 1} \quad (9.5)$$

$$L_w = \frac{R_{Ew}}{2\pi f_w Q_w} \quad C_w = \frac{Q_w}{2\pi f_w R_{Ew}} \quad L_{m1} = \frac{R_{Em}}{2\pi f_{m1} Q_{m1}} \quad C_{m1} = \frac{Q_{m1}}{2\pi f_{m1} R_{Em}} \quad (9.6)$$

$$L_{m2} = \frac{R_{Em}}{2\pi f_{m2} Q_{m2}} \quad C_{m2} = \frac{Q_{m2}}{2\pi f_{m2} R_{Em}} \quad L_t = \frac{R_{Et}}{2\pi f_t Q_t} \quad C_t = \frac{Q_t}{2\pi f_t R_{Et}} \quad (9.7)$$

# Pasívna výhybka 3. rádu

• ...

$$C_1 = \frac{1}{3\pi f_c R_E} \quad C_2 = 3C_1 \quad L = \frac{3R_E}{8\pi f_c}$$

$$L_2 = \frac{R_E}{4\pi f_c} \quad L_1 = 3L_2 \quad C = \frac{2}{3\pi f_c R_E}$$

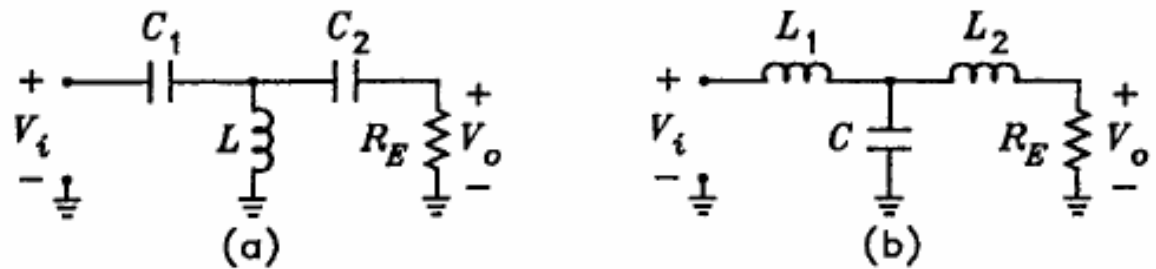


Figure 9.4: Third-order (a) high-pass and (b) low-pass filters.

# Návrh odporového deliča na vyrovnanie citlivosti reproduktorov

Figure 9.5(a) illustrates an L-pad connected to a driver. In Fig. 9.5(b), the driver is modeled by its voice-coil resistance  $R_E$ . For a desired voltage gain  $k_{\text{pad}} = V_2/V_1$  and input resistance  $R_{\text{in}}$ , the L-pad elements are given by

$$R_2 = \frac{R_{\text{in}} R_E}{(R_E/k_{\text{pad}}) - R_{\text{in}}} \quad R_1 = R_{\text{in}} - R_2 \parallel R_E \quad (9.10)$$

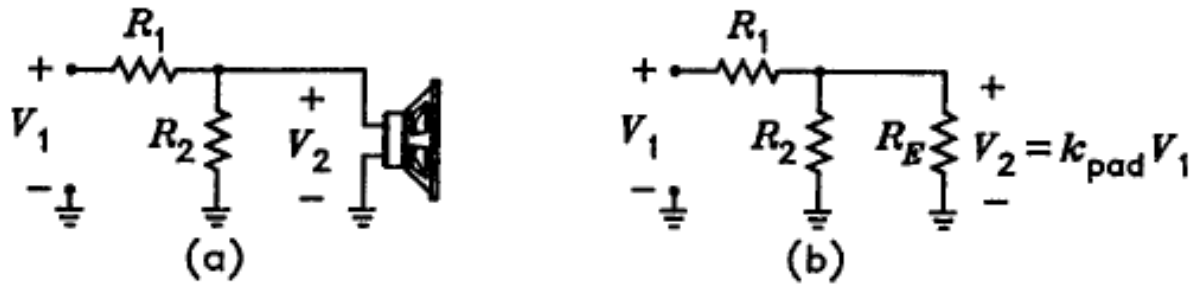


Figure 9.5: (a) L-pad and driver. (b) L-pad with the driver modeled by its voice-coil resistance  $R_E$ .

$$k_{\text{pad}} = \frac{p_{\text{sens1}}^{1V}}{p_{\text{sens2}}^{1V}} = \sqrt{\frac{R_{E2}}{R_{E1}} \times \frac{\eta_{01}}{\eta_{02}}} \quad k_{\text{pad}} = 10^{(SPL_{\text{sens1}}^{1V} - SPL_{\text{sens2}}^{1V})/20} = \sqrt{\frac{R_{E2}}{R_{E1}}} 10^{(SPL_{\text{sens1}}^{1W} - SPL_{\text{sens2}}^{1W})/20}$$

# Návrh odporového deliča na vyrovnanie citlivosti reproduktorov

- odporový delič slúži na vyrovnanie citlivosti reproduktorov
- zapája sa na vstup reproduktora s vyššou citlivosťou – cieľom je znížiť napätie na jeho vstupe

$$R_1 = R_{in} - \frac{R_2 R_{EVC}}{R_2 + R_{EVC}}$$

$$R_2 = \frac{R_{in} R_{EVC} k_{pad}}{R_{EVC} - R_{in} k_{pad}}$$

–

Suppose two drivers have the pressure sensitivities  $p_{sens1}^{1V}$  and  $p_{sens2}^{1V}$ , where  $p_{sens1}^{1V} < p_{sens2}^{1V}$ , the efficiencies  $\eta_{01}$  and  $\eta_{02}$ , and the voice-coil resistances  $R_{E1}$  and  $R_{E2}$ . The value of  $k_{pad}$  for a L-pad in series with driver 2 to make it have the same effective  $p_{sens}^{1V}$  as driver 1 is given by

$$k_{pad} = \frac{p_{sens1}^{1V}}{p_{sens2}^{1V}} = \sqrt{\frac{R_{E2}}{R_{E1}} \times \frac{\eta_{01}}{\eta_{02}}} \quad (9.11)$$

If the *SPL* sensitivities of the drivers are given, the value of  $k_{pad}$  is

$$k_{pad} = 10^{(SPL_{sens1}^{1V} - SPL_{sens2}^{1V})/20} = \sqrt{\frac{R_{E2}}{R_{E1}}} 10^{(SPL_{sens1}^{1W} - SPL_{sens2}^{1W})/20} \quad (9.12)$$



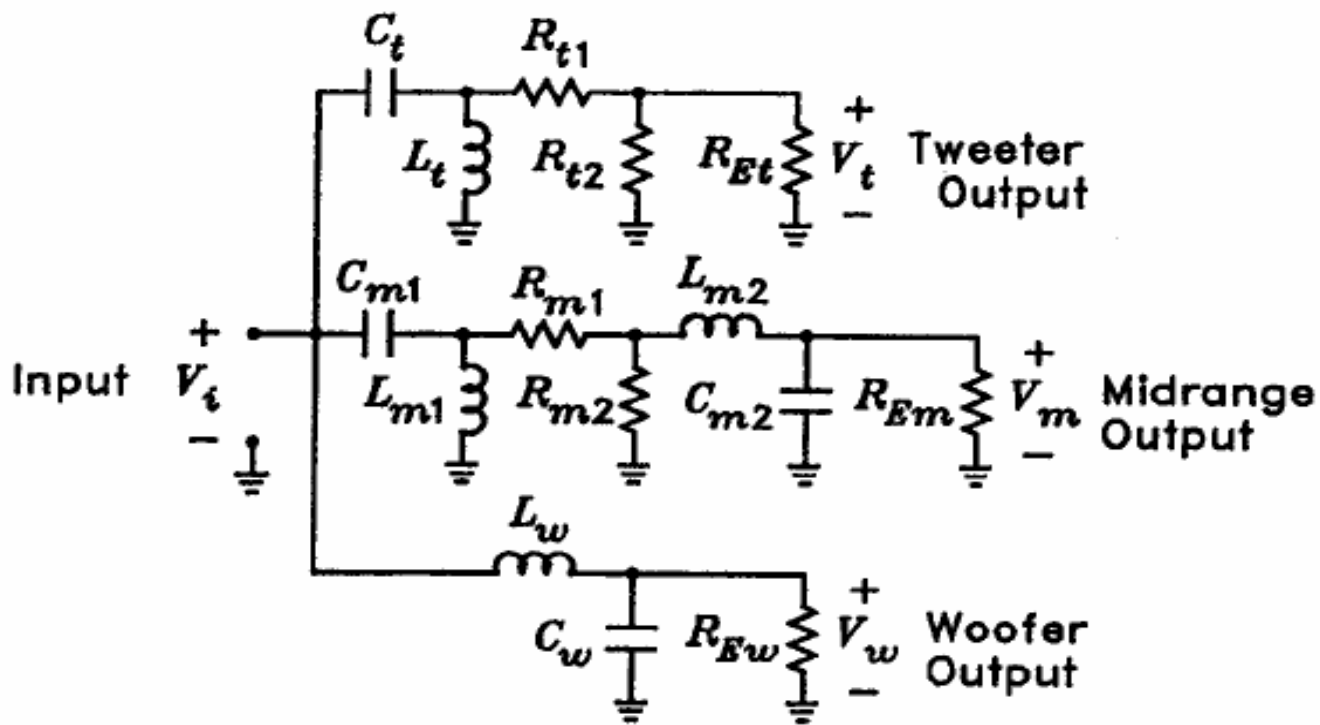


Figure 9.6: Example crossover network with two L-pads.

# Kompenzácia vstupnej impedancie

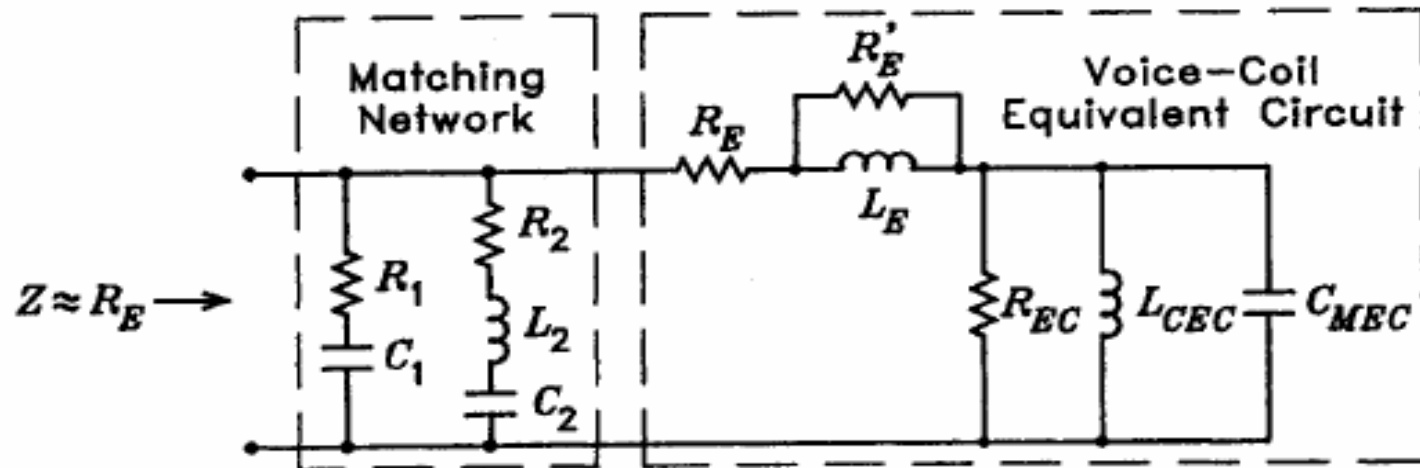


Figure 9.7: Voice-coil equivalent circuit with matching networks.

In order for the input impedance to the network plus the driver to be equal to  $R_E$  at all frequencies, the matching network elements are given by

$$R_1 = R_E \left( 1 + \frac{R_E}{R'_E} \right) \quad C_1 = \frac{L_E}{R_E^2} \quad (9.15)$$

$$R_2 = R_E \left( 1 + \frac{Q_{EC}}{Q_{MC}} \right) \quad C_2 = \frac{1}{2\pi f_C R_E Q_{EC}} \quad L_2 = \frac{R_E Q_{EC}}{2\pi f_C} \quad (9.16)$$

where  $f_C$  is the closed-box resonance frequency. These equations are derived under the assumption that  $C_1$  is an open circuit in the low-frequency range where  $R_2$ ,  $C_2$ , and  $L_2$  are active and that  $L_2$  is an open circuit in the high-frequency range where  $R_1$  and  $C_1$  are active. Because  $L_E$  and  $R'_E$  are not frequency independent in general, the values of  $R_1$  and  $C_1$  might be determined from the values of  $L_E$  and  $R'_E$  at the desired crossover frequency.

## 9.5 Effect of the Driver Phase Response

A loudspeaker system should be designed so that phase cancellation cannot occur in the on-axis pressure caused by two drivers operating out of phase at the crossover frequency. To explain this

## 9.6 Constant-Voltage and All-Pass Functions

Crossover networks are often designed to satisfy either a constant-voltage condition or an all-pass condition. To see how these are derived, let  $p = s/\omega_0$  be the normalized frequency. Let  $D_n(p)$  be a  $n$ th-order polynomial in  $p$  of the form

$$D_n(p) = 1 + a_1p + a_2p^2 + \cdots + p^n \quad (9.17)$$

The transfer functions of  $n$ th order low-pass and high-pass filters can be written

$$T_{LP}(p) = \frac{1}{D_n(p)} \quad T_{HP}(p) = \frac{p^n}{D_n(p)} \quad (9.18)$$

We wish to investigate the conditions for which

$$|T_{LP}(ju) \pm T_{HP}(ju)| = 1 \quad (9.19)$$

where  $u = \omega/\omega_0$  and the minus sign represents a reversal of the polarity of the high-frequency driver to the network. Networks which satisfy this condition are called all-pass networks. In the case that  $T_{LP}(p) + T_{HP}(p) = 1$ , the network is called a constant-voltage network.

The generation of all-pass transfer functions requires factorization of the polynomial  $1 + p^n$  into the product of first and second-order polynomials having real coefficients. For  $n = 1$ , the polynomial is already factored. The factored polynomials for the cases  $2 \leq n \leq 4$  are as follows:

$$1 + p^2 = (1 + p)(1 - p) \quad 1 + p^3 = (1 + p)(1 - p + p^2) \quad (9.20)$$

$$1 + p^4 = (1 + \sqrt{2}p + p^2)(1 - \sqrt{2}p + p^2) \quad (9.21)$$

The denominator polynomial  $D_n(p)$  is obtained by taking the factors of  $1 + p^n$ , changing the signs of all negative coefficients of  $p$ , and multiplying the factors. It follows that

$$D_2(p) = (1 + p)^2 \quad D_3(p) = (1 + p)(1 + p + p^2) \quad D_4(p) = (1 + \sqrt{2}p + p^2)^2 \quad (9.22)$$

It is straightforward to obtain orders higher than 4 by factoring the  $1 + p^n$  polynomial. The only cases which cannot be used are those for which a factor is  $(1 + p^2)$ . This would result in complex poles on the  $j\omega$  axis, thus causing oscillations. For example, this occurs with  $1 + p^6$ .

### First Order

For  $n = 1$ , we have

$$T_{LP}(p) = \frac{1}{1 + p} \quad T_{HP}(p) = \frac{p}{1 + p} \quad T_{LP}(p) \pm T_{HP}(p) = \frac{1 \pm p}{1 + p} \quad (9.23)$$

It is obvious that  $T_{LP}(p) + T_{HP}(p) = 1$ , so that the first-order crossover is constant voltage. This is the only order for which the network is constant voltage. For  $p = ju$ , the magnitude of the difference is

$$|T_{LP}(ju) - T_{HP}(ju)| = \left| \frac{1 - ju}{1 + ju} \right| = \frac{\sqrt{1 + u^2}}{\sqrt{1 + u^2}} = 1 \quad (9.24)$$

Thus the first-order function is all-pass if the difference connection is used.

At the crossover frequency, i.e. for  $p = j1$ ,  $T_{LP}(j1) = 1/\sqrt{2} \angle -45^\circ$  and  $T_{HP}(j1) = 1/\sqrt{2} \angle 45^\circ$ . The angle between the phasors is  $90^\circ$ . If crossover occurs near the resonance frequency of the high-frequency driver, its phase shift causes the phase difference to be greater than  $90^\circ$  for the sum connection and less than  $90^\circ$  for the difference connection. To prevent phase cancellation, the difference connection is the proper one.

## Second Order

For  $n = 2$ , we have

$$T_{LP}(p) = \frac{1}{(1+p)^2} \quad T_{HP}(p) = \frac{p^2}{(1+p)^2} \quad T_{LP}(p) \pm T_{HP}(p) = \frac{1 \pm p^2}{(1+p)^2} \quad (9.25)$$

For  $p = j1$ , i.e. for  $\omega = \omega_0$ , it is obvious that the sum connection exhibits a null. For the difference connection, the numerator can be factored to obtain  $(1+p)(1-p)$ . For  $p = ju$ , we have

$$|T_{LP}(ju) - T_{HP}(ju)| = \left| \frac{(1 - ju)(1 + ju)}{(1 + ju)^2} \right| = \left| \frac{1 - ju}{1 + ju} \right| = 1 \quad (9.26)$$

Thus the difference connection is all-pass.

At the crossover frequency, i.e. for  $p = j1$ ,  $T_{LP}(j1) = 0.5 \angle -90^\circ$  and  $T_{HP}(j1) = 0.5 \angle 90^\circ$ . The angle between the phasors is  $180^\circ$  so that  $T_{LP}(j1) + T_{HP}(ju) = 0$ . For the difference connection, the angle between the phasors is  $0^\circ$  and  $T_{LP}(j1) - T_{HP}(j1) = 1 \angle 0^\circ$ . If crossover occurs near the resonance frequency of the high-frequency driver, its phase shift causes the phase difference to be between  $90^\circ$  and  $180^\circ$  for the sum connection and less than  $90^\circ$  for the difference connection. To prevent phase cancellation, the difference connection is the proper one.

### Third Order

For  $n = 3$ , we have

$$T_{LP}(p) = \frac{1}{(1+p)(1+p+p^2)} \quad T_{HP}(p) = \frac{p^3}{(1+p)(1+p+p^2)} \quad (9.27)$$

The sum and difference are

$$T_{LP}(p) \pm T_{HP}(p) = \frac{1 \pm p^3}{(1+p)(1+p+p^2)} = \frac{(1 \pm p)(1 \mp p + p^2)}{(1+p)(1+p+p^2)} \quad (9.28)$$

For the sum connection, the  $(1+p)$  factors cancel. For  $p = ju$ , the magnitude of the sum is

$$|T_{LP}(ju) + T_{HP}(ju)| = \left| \frac{1 - ju - u^2}{1 + ju - u^2} \right| = \frac{\sqrt{(1-u^2)^2 + u^2}}{\sqrt{(1-u^2)^2 + u^2}} = 1 \quad (9.29)$$

which is all-pass.

For the difference connection, the  $(1+p+p^2)$  factors cancel. For  $p = ju$ , the magnitude of the difference is

$$|T_{LP}(ju) - T_{HP}(ju)| = \left| \frac{1 - ju}{1 + ju} \right| = \frac{\sqrt{1+u^2}}{\sqrt{1+u^2}} = 1 \quad (9.30)$$

which is also all-pass. The first-order all-pass response of the difference connection results in less phase shift than that of the second-order all-pass response of the sum connection.

At the crossover frequency, i.e. for  $p = j1$ ,  $T_{LP}(j1) = 1/\sqrt{2} \angle -135^\circ$  and  $T_{HP}(j1) = 1/\sqrt{2} \angle 135^\circ$ . The angle between the phasors is  $90^\circ$ . If crossover occurs near the resonance frequency of the high-frequency driver, its phase shift causes the phase difference to be less than  $90^\circ$  for the sum connection and greater than  $90^\circ$  for the difference connection. To prevent phase cancellation, the sum connection is the proper one.



## 9.7 Active Crossover Networks

If a separate power amplifier is used for each driver in a system, the crossover networks can precede the power amplifiers. In this case, active operational amplifier filters can be used for the networks. A system which uses two amplifiers, one to drive the woofer and the other to drive both the midrange and the tweeter, is called a bi-amplified system. In bi-amplified systems, passive crossover networks are used to cross the midrange over to the tweeter while active networks are used to cross the woofer over to the combination midrange and tweeter. A system which uses three amplifiers, one each for the woofer, midrange, and the tweeter, is called a tri-amplified system. In this case, active crossover networks are used for all three drivers.

One of the most common filter topologies used in active crossover networks is the Sallen-Key filter. The networks described in this section are the Sallen-Key low-pass and high-pass filters. Band pass filters can be realized by cascading a high-pass filter with a low-pass filter.

## Second Order

Figure 9.14(a) shows the diagram of a second-order Sallen-Key low-pass filter with unity voltage gain in its passband. This filter has the transfer function

$$\frac{V_{ol}}{V_i} = \frac{1}{(s/\omega_1)^2 + (1/Q_1)(s/\omega_1) + 1} \quad (9.37)$$

where  $\omega_1$  is the radian resonance frequency and  $Q_1$  is the quality factor. Let  $\omega_1 = 2\pi f_1$ ,  $Q_1$ ,  $R_1$  and  $R_2$  be specified. The values of  $C_1$  and  $C_2$  are given by

$$C_1 = \frac{Q_1}{2\pi f_1} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \quad C_2 = \frac{1}{2\pi f_1 (R_1 + R_2) Q_1} \quad (9.38)$$

The filter is often designed with  $R_1 = R_2$ .

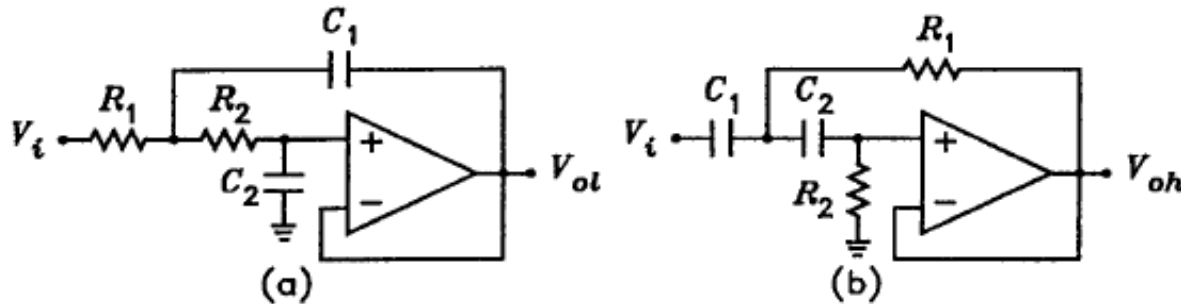


Figure 9.14: Second-order Sallen-Key (a) low-pass and (b) high-pass filters.

Figure 9.14(b) shows the circuit diagram of a second-order Sallen-Key high-pass filter with unity

voltage gain in its passband. This filter has the transfer function

$$\frac{V_{oh}}{V_i} = \frac{(s/\omega_2)^2}{(s/\omega_2)^2 + (1/Q_2)(s/\omega_2) + 1} \quad (9.39)$$

where  $\omega_2$  is the radian resonance frequency and  $Q_2$  is the quality factor. Let  $\omega_2 = 2\pi f_2$ ,  $Q_2$ ,  $C_1$  and  $C_2$  be specified. The values of  $R_1$  and  $R_2$  are given by

$$R_1 = \frac{1}{2\pi f_2 Q_2 (C_1 + C_2)} \quad R_2 = \frac{Q_2}{2\pi f_2} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \quad (9.40)$$

The filter is often designed with  $C_1 = C_2$ .

The second-order networks are usually designed with  $f_1 = f_2$  and  $Q_1 = Q_2 = 0.5$ . This makes the difference between the low-pass and the high-pass functions a second-order all-pass transfer function. For  $Q = 0.5$ , the  $-6$  dB cutoff frequency of each filter is equal to its resonance frequency. At the resonance frequency, the voltage output of the low-pass filter is lagging by  $90^\circ$  and the voltage output of the high-pass filter is leading by  $90^\circ$ . The phase difference between the voltage outputs is  $180^\circ$  at all frequencies. To minimize phase cancellation at the crossover frequency, the voice coil of one of the drivers should usually be connected with its polarity reversed compared to the voice coil polarity of the other driver.

### Third Order

Figure 9.15 shows the diagrams of third-order Sallen-Key low-pass and high-pass filters with unity gain in the passbands. These filters are usually designed to have Butterworth responses with equal  $-3$  dB cutoff frequencies. In this case, the sum of the high-pass and low-pass transfer functions is a second-order all-pass function while the difference is a first-order all-pass function. At the  $-3$  dB cutoff frequency, the output of the low-pass filter is lagging by  $135^\circ$  and the output of the high-pass filter is leading by  $135^\circ$ . The phase difference between the two filter outputs is  $90^\circ$  at all frequencies. To minimize phase cancellation at the crossover frequency, the voice coils of the two drivers should usually be connected with the same polarity.

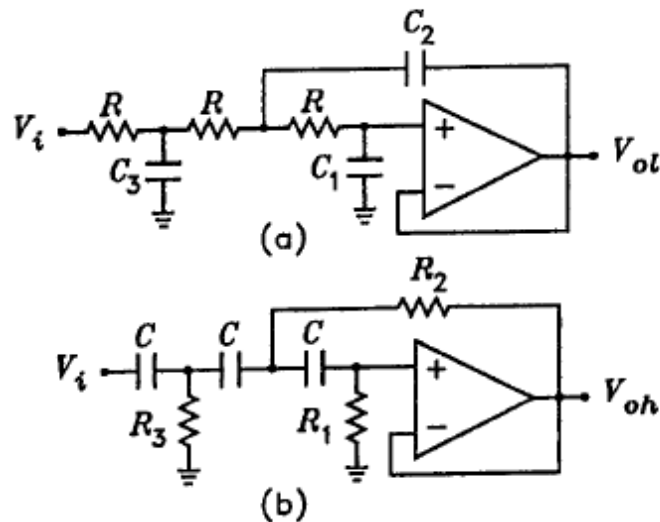


Figure 9.15: Third-order Sallen-Key (a) low-pass and (b) high-pass filters.

Let  $f_c$  be the  $-3$  dB cutoff frequency for the two Butterworth third-order filters. The design

equations for the capacitors in the low-pass filter and the resistors in the high-pass filter are

$$C_1 = \frac{0.20245}{2\pi f_c R} \quad C_2 = \frac{3.5465}{2\pi f_c R} \quad C_3 = \frac{1.3926}{2\pi f_c R} \quad (9.41)$$

$$R_1 = \frac{4.93949}{2\pi f_c C} \quad R_2 = \frac{0.28194}{2\pi f_c C} \quad R_3 = \frac{0.71808}{2\pi f_c C} \quad (9.42)$$